

コードとデザイン

東京藝術大学 芸術情報センター開設科目 金曜4-5限 第5週

2025.05.09 松浦知也 (matsura.tomoya@noc.geidai.ac.jp teach@matsuuratomoya.com)



本日のスケジュール

- Unconventional Computingの紹介（15分）
- ロジック回路の組み合わせと加算器の作り方（20分）
- NAND回路を作ってみよう
- NAND回路を組み合わせで全加算器を作ろう


Unconventional Computing

Peter Vogel



<https://www.youtube.com/watch?v=NlixUuoDrHw>

Eirik Brandal

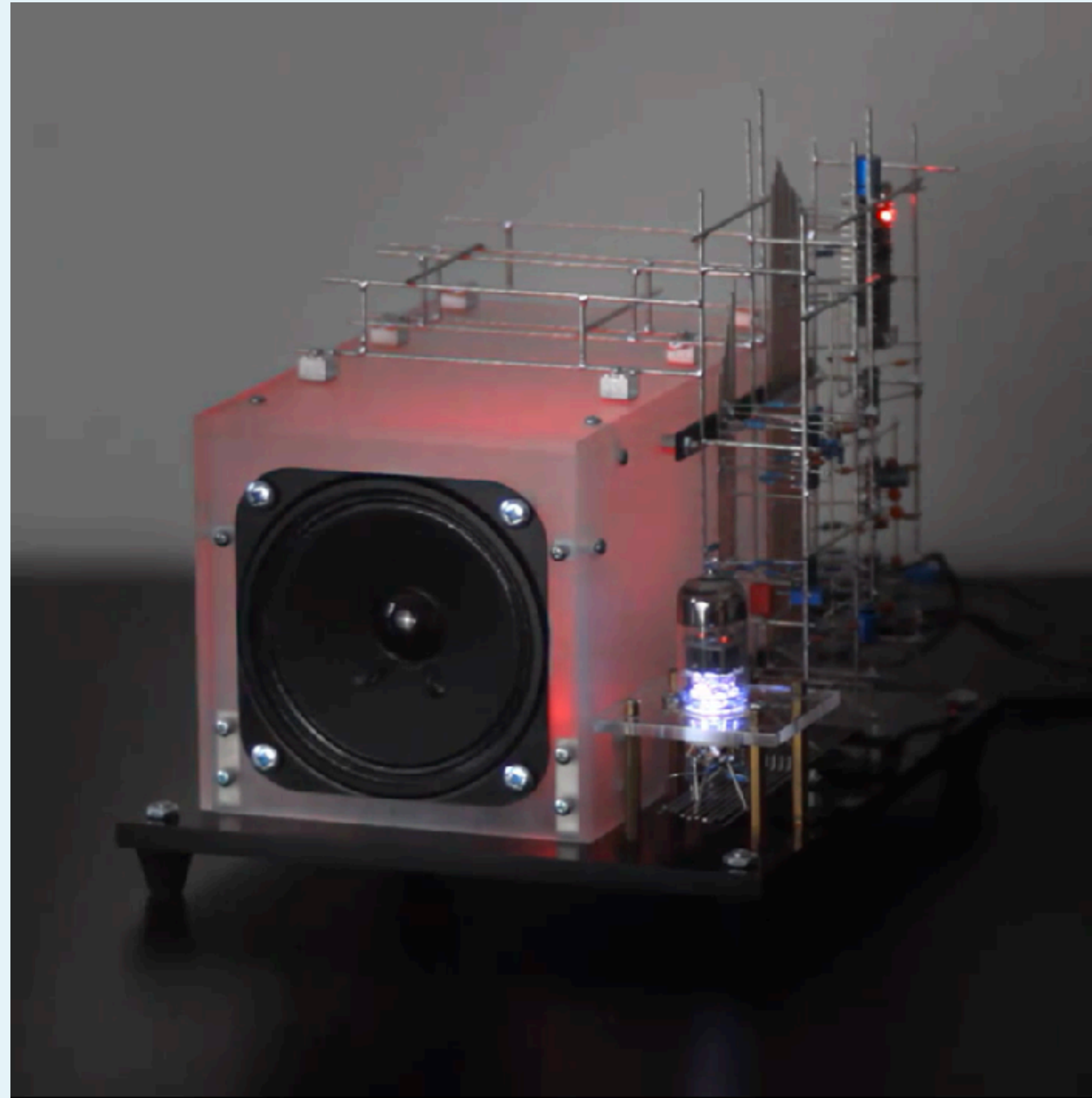

<https://www.instagram.com/p/CYmRmb5hWAX/>

活線プロジェクト（ひつじ）



<https://github.com/tenari-jp/electrical-Ikebana>

1 Bit 1Hz CPU(CW&T)







<https://vimeo.com/58737613>



Domino Addition - Numberphile(2012)
<https://www.youtube.com/watch?v=INuPy-r1GuQ>



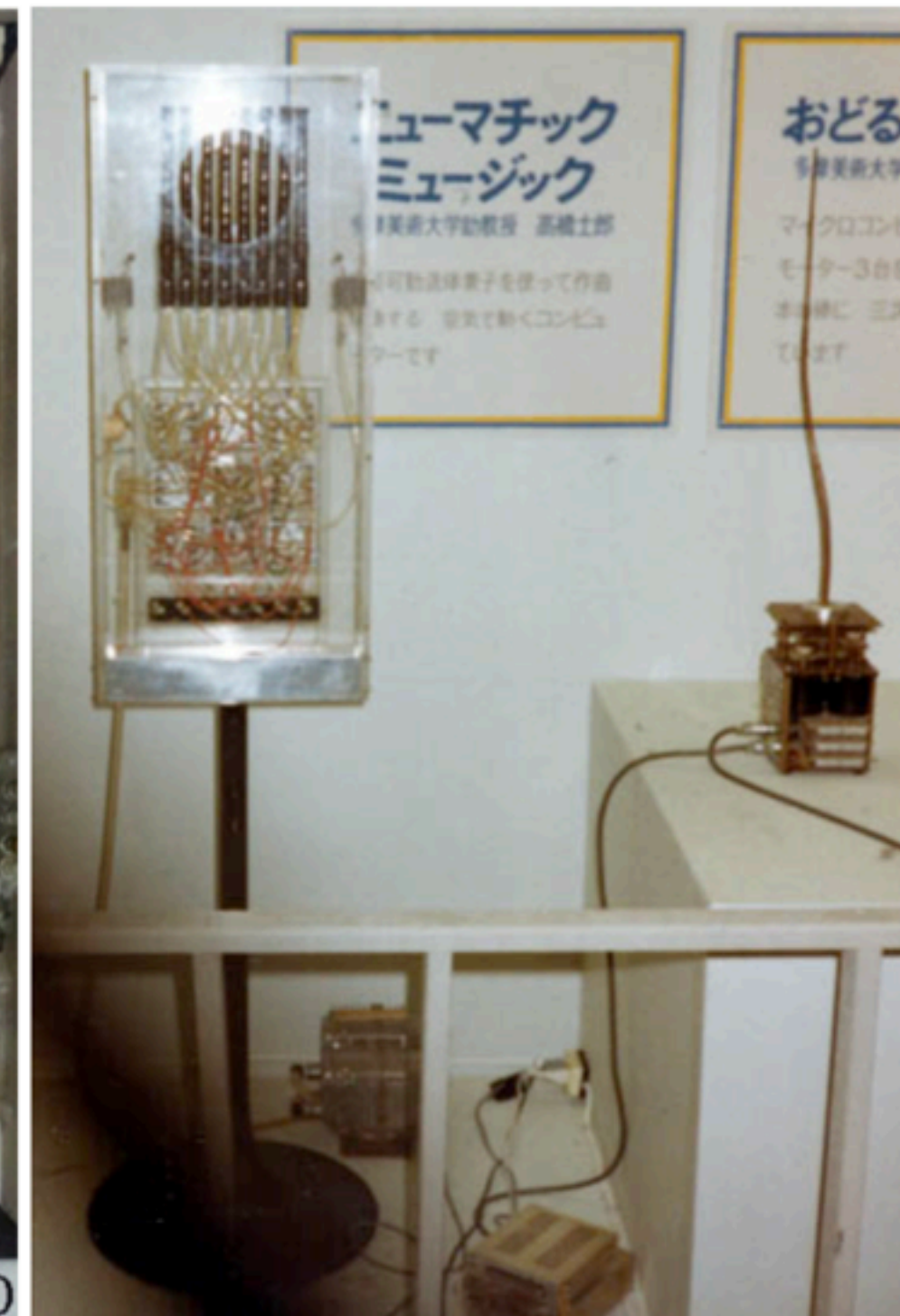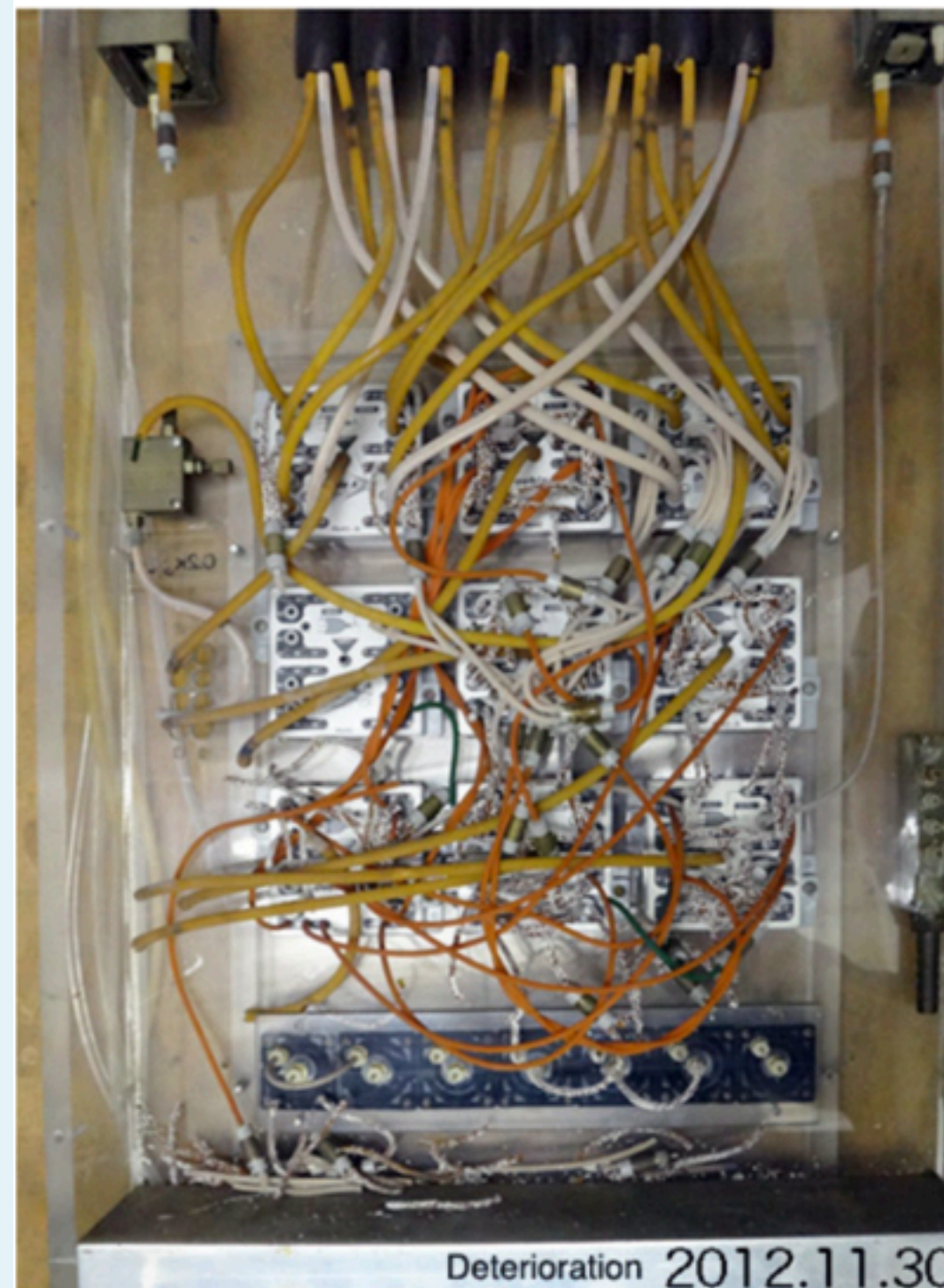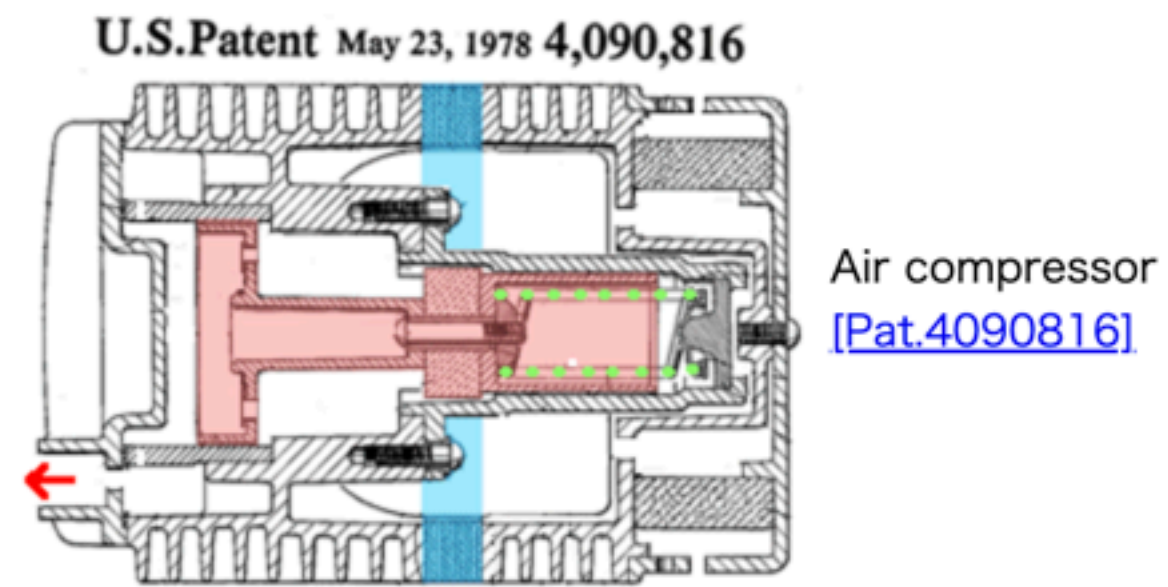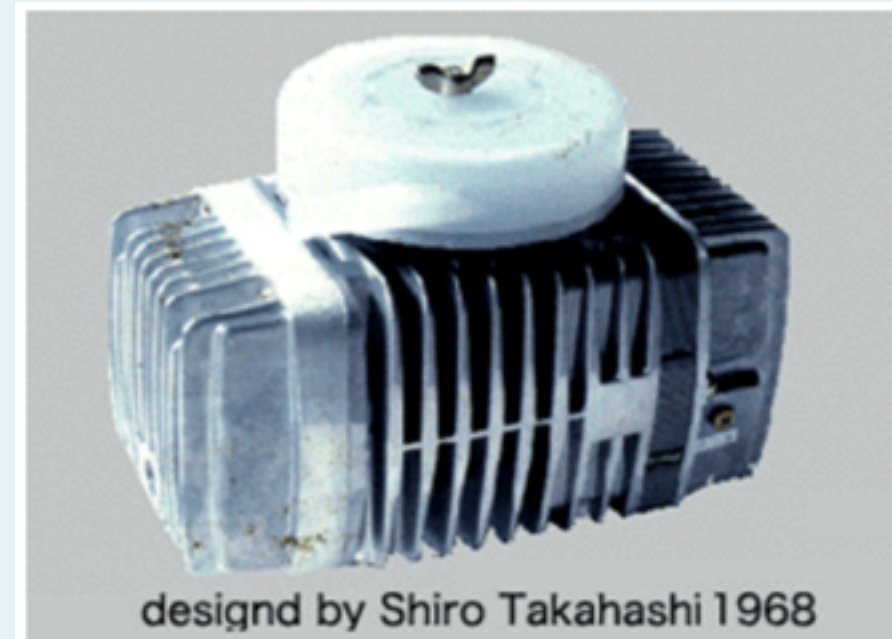
<https://youtube.com/watch?v=IxXaizglscw>



“ニューマチック コンピューター” 高橋士郎 (1970)

<http://www.shiro1000.jp/mpu/compo.htm>
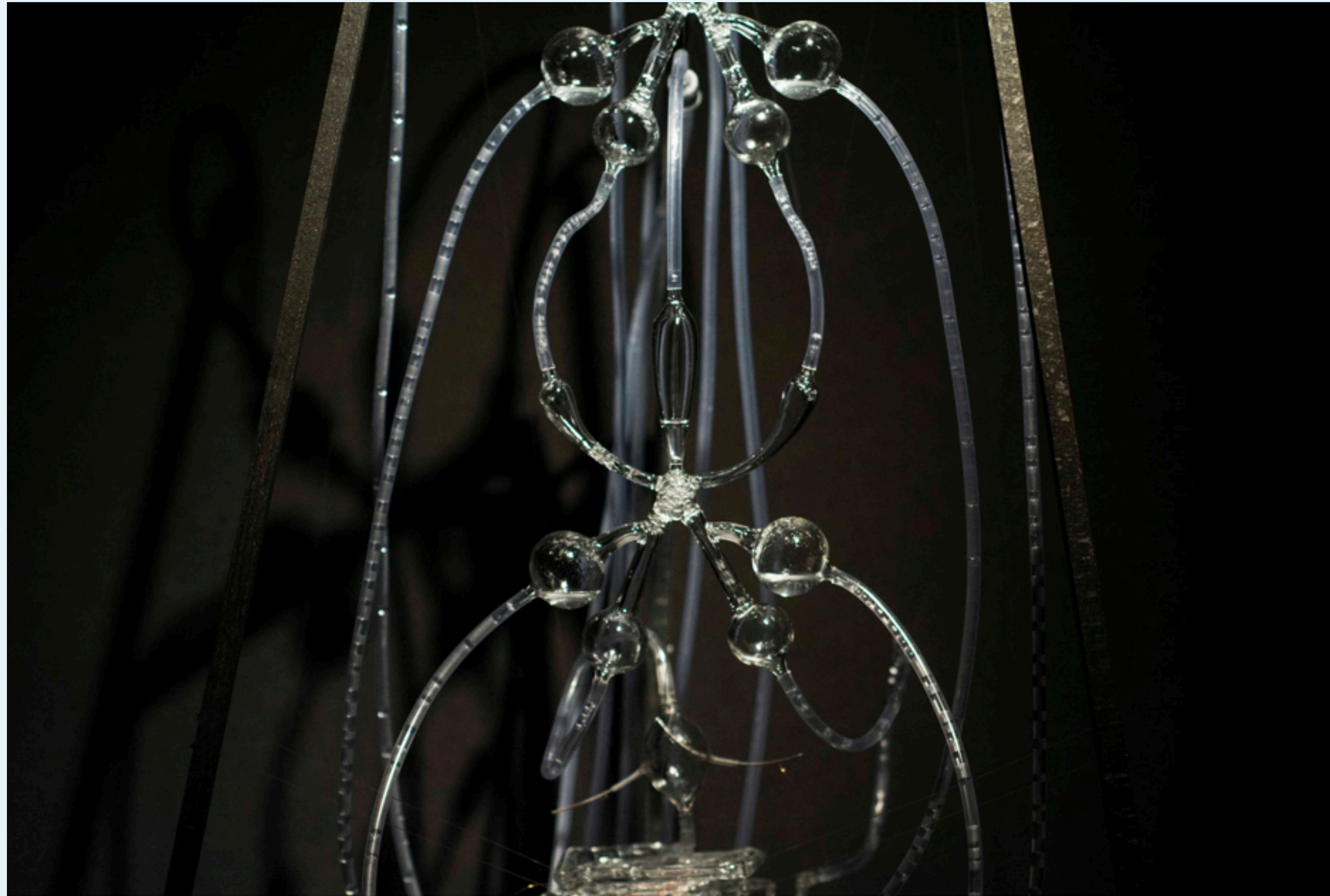
<https://mediaarts-db.bunka.go.jp/id/M781436>



"Fluid Memory" Ioana Vreme Moser (2019-2020)

<https://www.ioanavrememoser.com/fluidmemory>



“PISS (ON) LOGIC”, MARTIN HOWSE & JONATHAN KEMP(2015)

<https://vimeo.com/172568522>


<https://projects.stwst.at/stwst48/pissonlogic-by-martin-howse-and-jonathan-kemp/index.html>



<https://ja.wikipedia.org/wiki/酒船石遺跡>

酒船石が流体素子であった可能性に関する考察(2017),村上優依・窪田佳寛・望月修

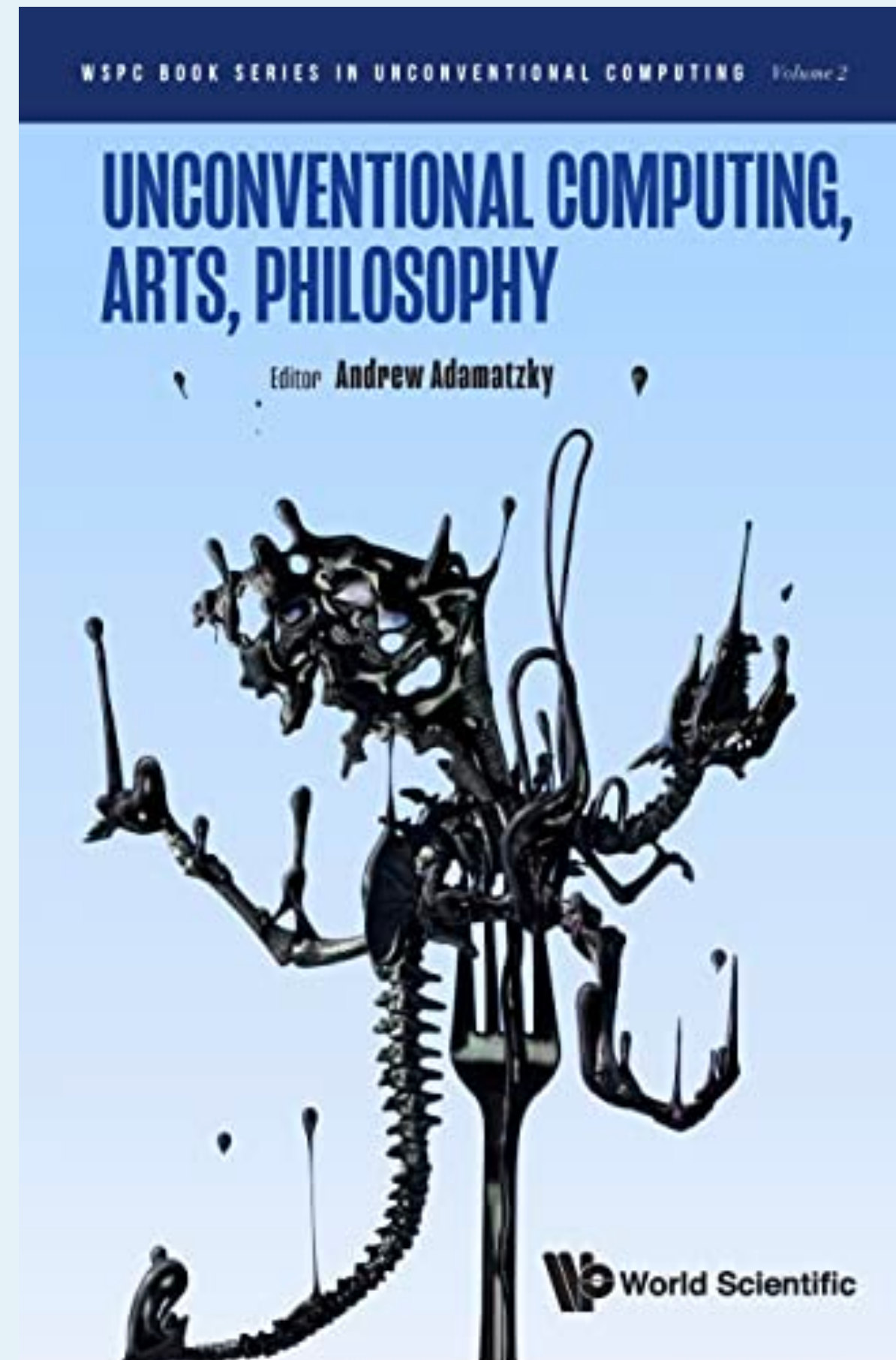https://www.nagare.or.jp/download/noauth.html?d=36-6_tokushu13.pdf&dir=63



Unconventional Computing, Arts, Philosophy (Unconventional Computing, 2),
Edited by Andrew Adamatzky, 2022, World Scientific Pub Co Inc

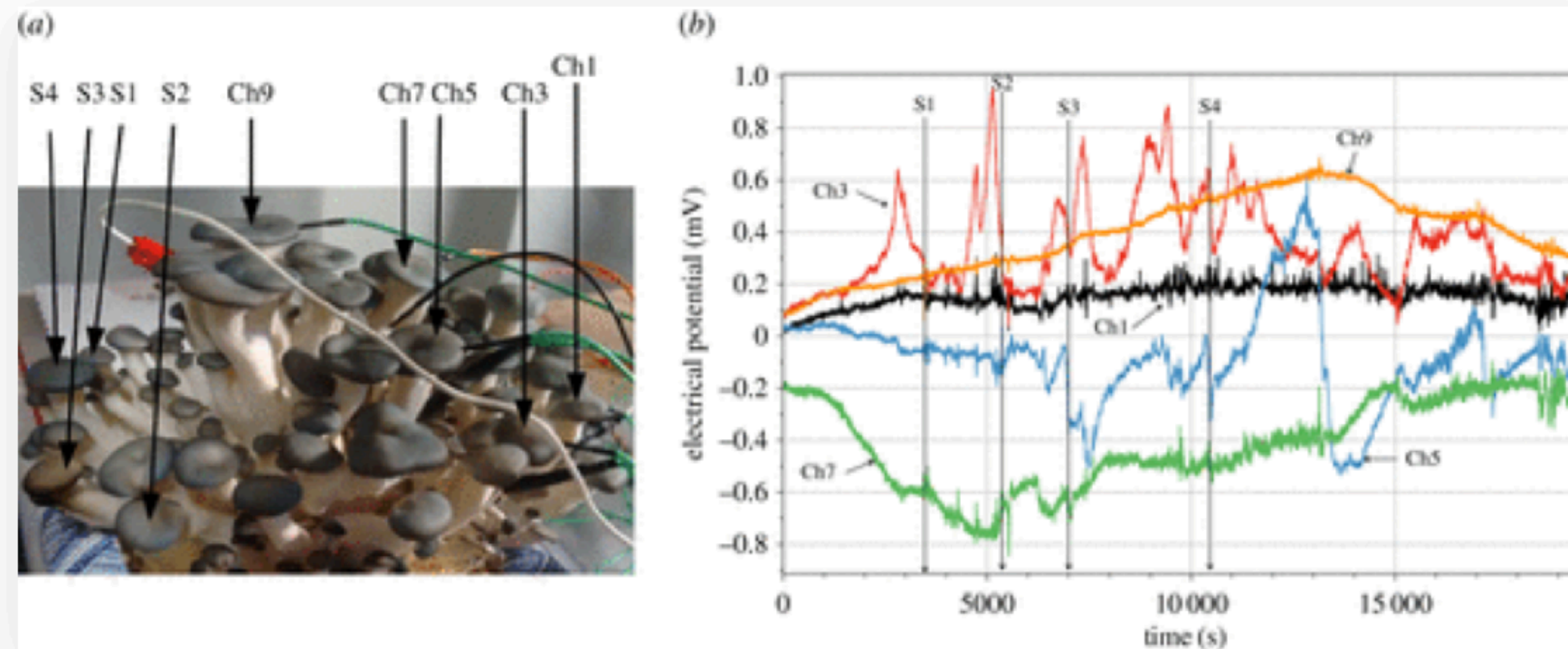


Figure 4. Stimulation of fruits. (a) Set-up of recording, sites of stimulation and location of electrode pairs corresponding to channels Ch1–Ch9. (b) Electrical potential recording on five mushrooms. Channel Ch1 is shown by black, Ch3 red, Ch5 blue, Ch7 green and Ch9 orange. The following stimuli have been applied to fruiting bodies. (S1) 3450 s: start open flame stimulation for 20 s. (S2) 5310 s: start open flame stimulation for 60 s. (S3) 7000 s: ethanol drop is placed on a cap of the fruit. (S4) 10440 s: 15 mg of table salt is placed on a cap of one of fruiting bodies.

"Towards fungal computer", Adamatzky Andrew, (2018), *Interface Focus*.8,2018002920180029
<http://doi.org/10.1098/rsfs.2018.0029>

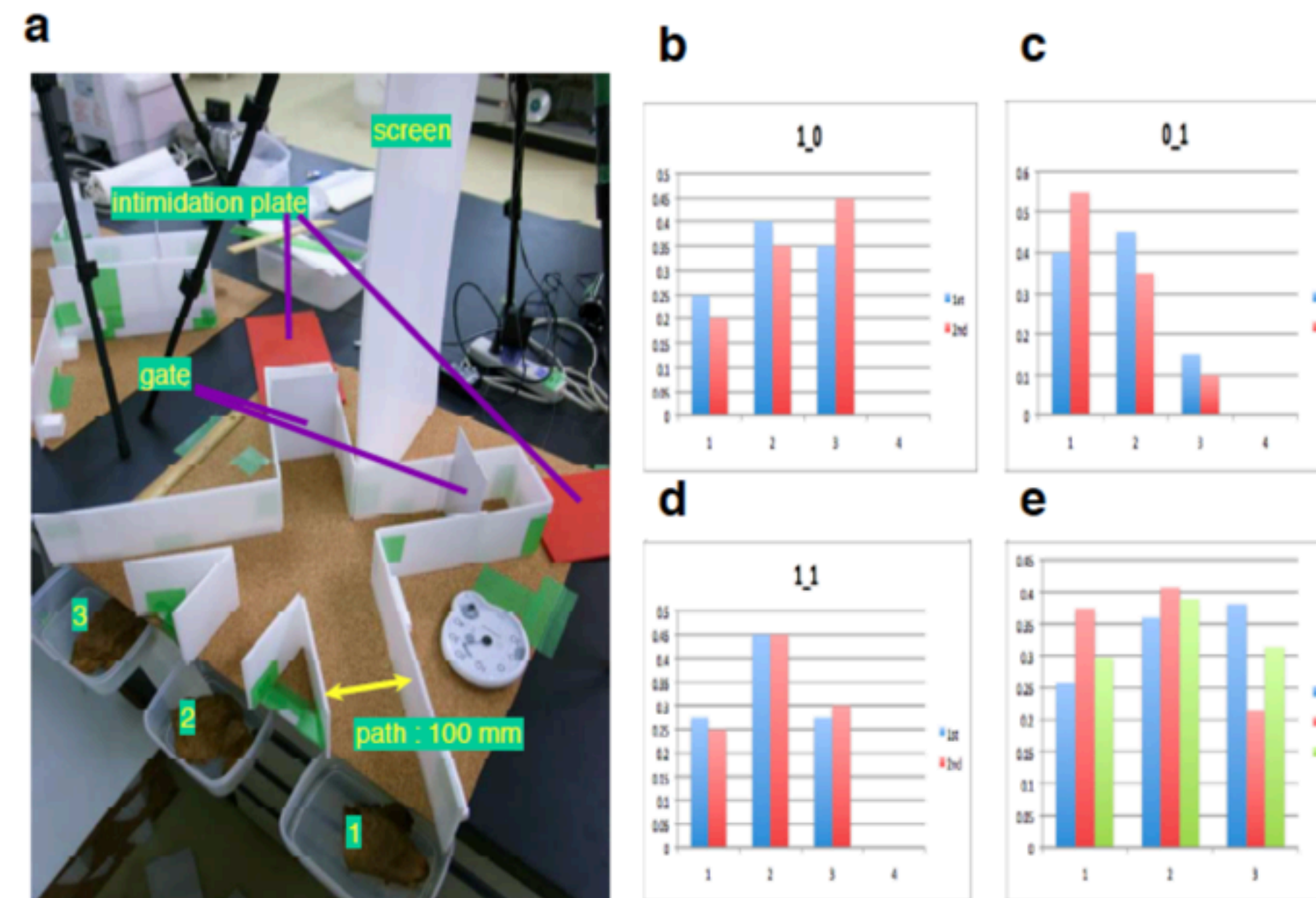


FIGURE 5. a. Implementation of AND gate by real soldier crabs. A or B represents input space for input x or y , respectively. The symbol 1, 2 and 3 represent output for $\text{NOT}(x) \text{ AND } y$, $x \text{ AND } y$, and $x \text{ AND NOT}(y)$, respectively. The experimental results of AND gate implemented by real soldier crabs. b. Frequency distribution of output 1, 2 and 3 for input, (1, 0). Output 4 represents the rate of individuals not reaching the output in a limited time. c. Frequency distribution for input, (0, 1). d. Frequency distribution for input, (1, 1). e. Frequency distribution of output 1, 2 and 3 over 21 trials.

“Robust Soldier Crab Ball Gate” Yukio-Pegio Gunji, Yuta Nishiyama, Andrew Adamatzky(2012)
<https://arxiv.org/abs/1204.1749>

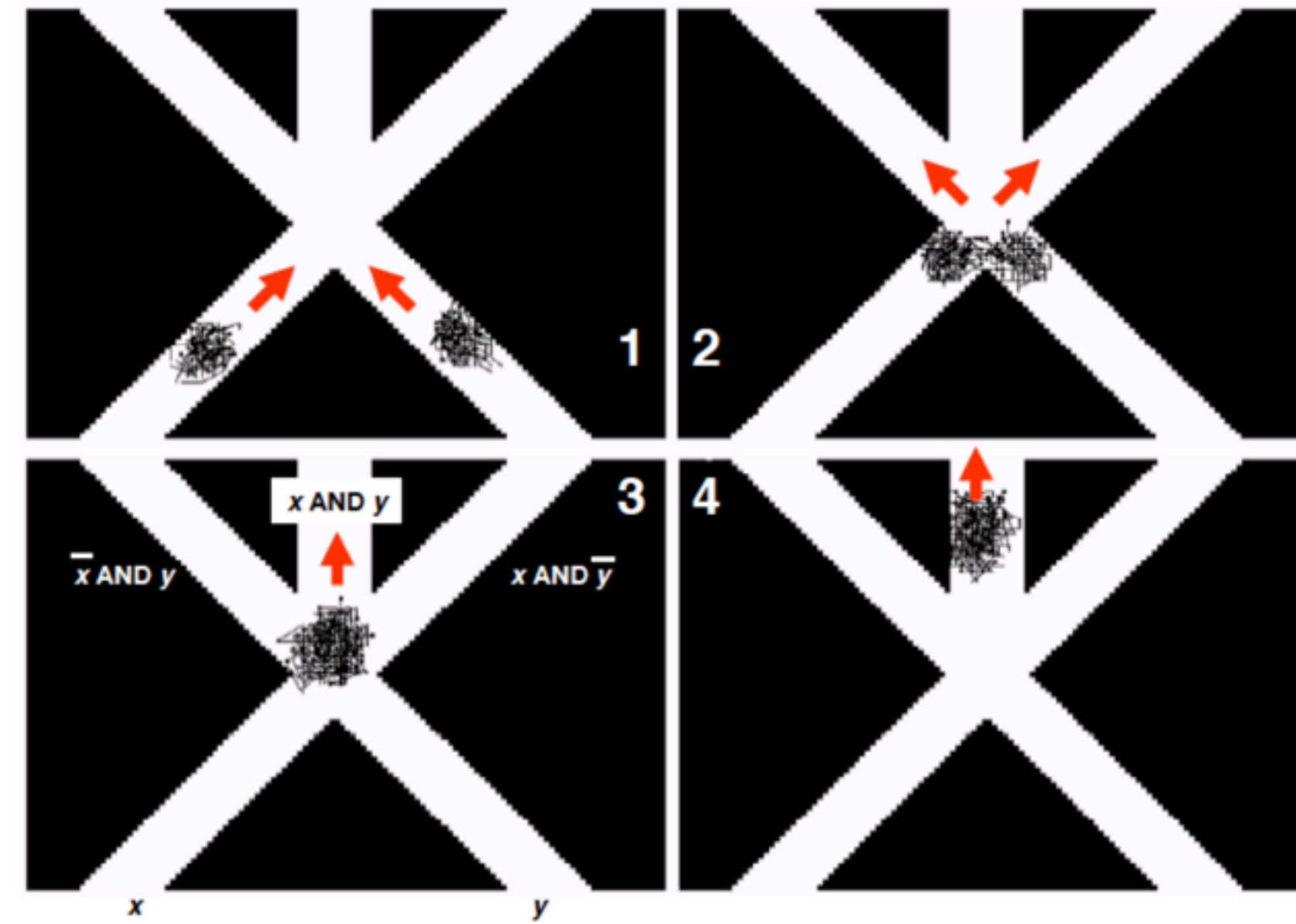


FIGURE 3. A series of snap shots (1, 2, 3 and 4) in AND gate of swarm balls. A swarm ball locate at x - and y -position consists of 40 agents, respectively. Each agent is represented by a square with its 5-steps-trajectories. Red arrows represent the direction of motion of a swarm ball.



“Dr.Stone(24)” 原作：稲垣理一郎、作画：Boichi、2022、21p




<https://ja.wikipedia.org/wiki/%E3%83%91%E3%83%A9%E3%83%A1%E3%83%88%E3%83%AD%E3%83%B3>


NANDゲートを作ろう


必要パーツ

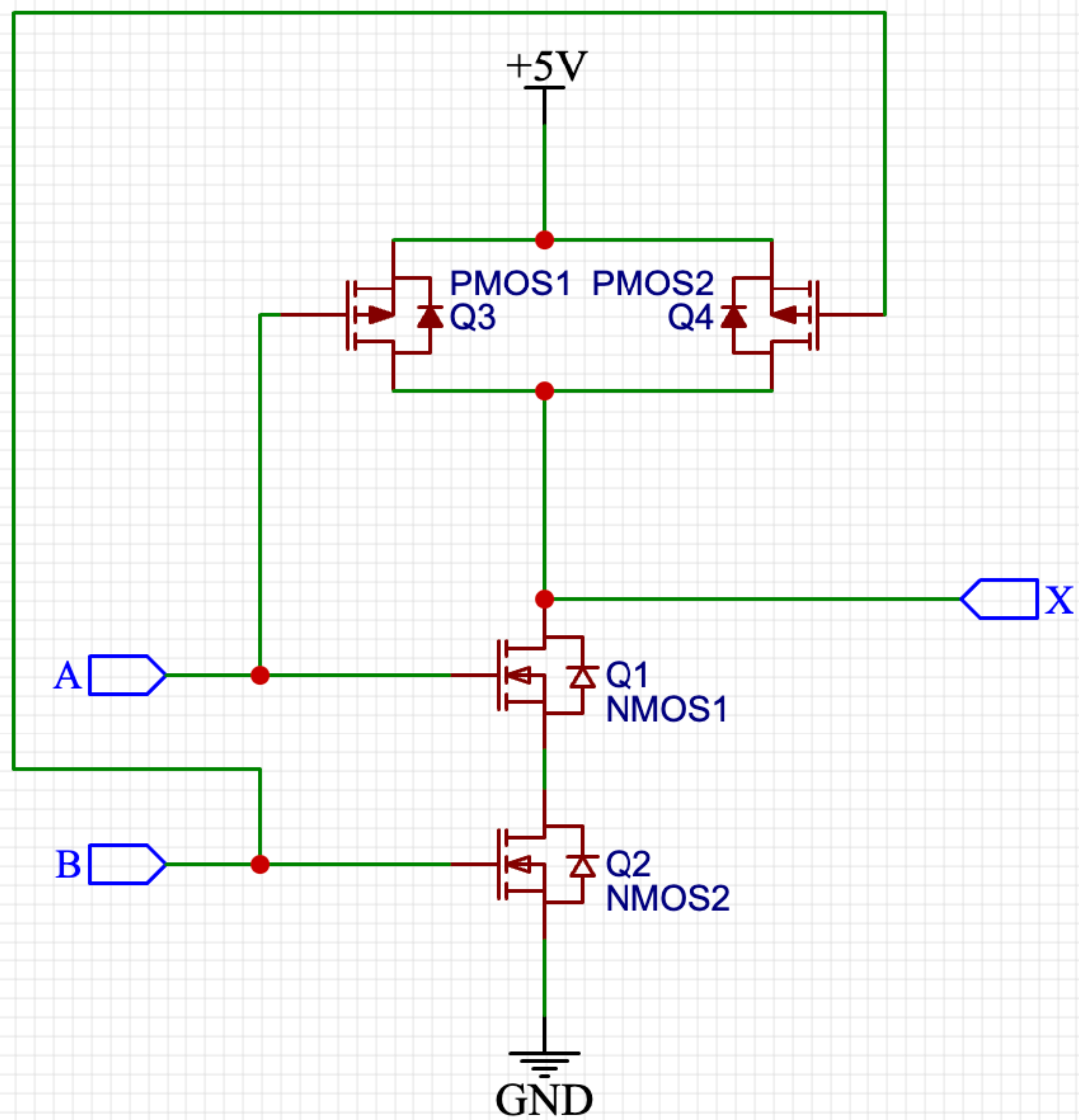
- ボタン電池(3V) or 9V電池x1
- 銅箔テープ
- N型MOSFET(2SK4017) x2
- P型MOSFET (MTP4835) x2
- 抵抗入りLEDx1




この部分がどうしても他の線を跨ぐので工夫しよう

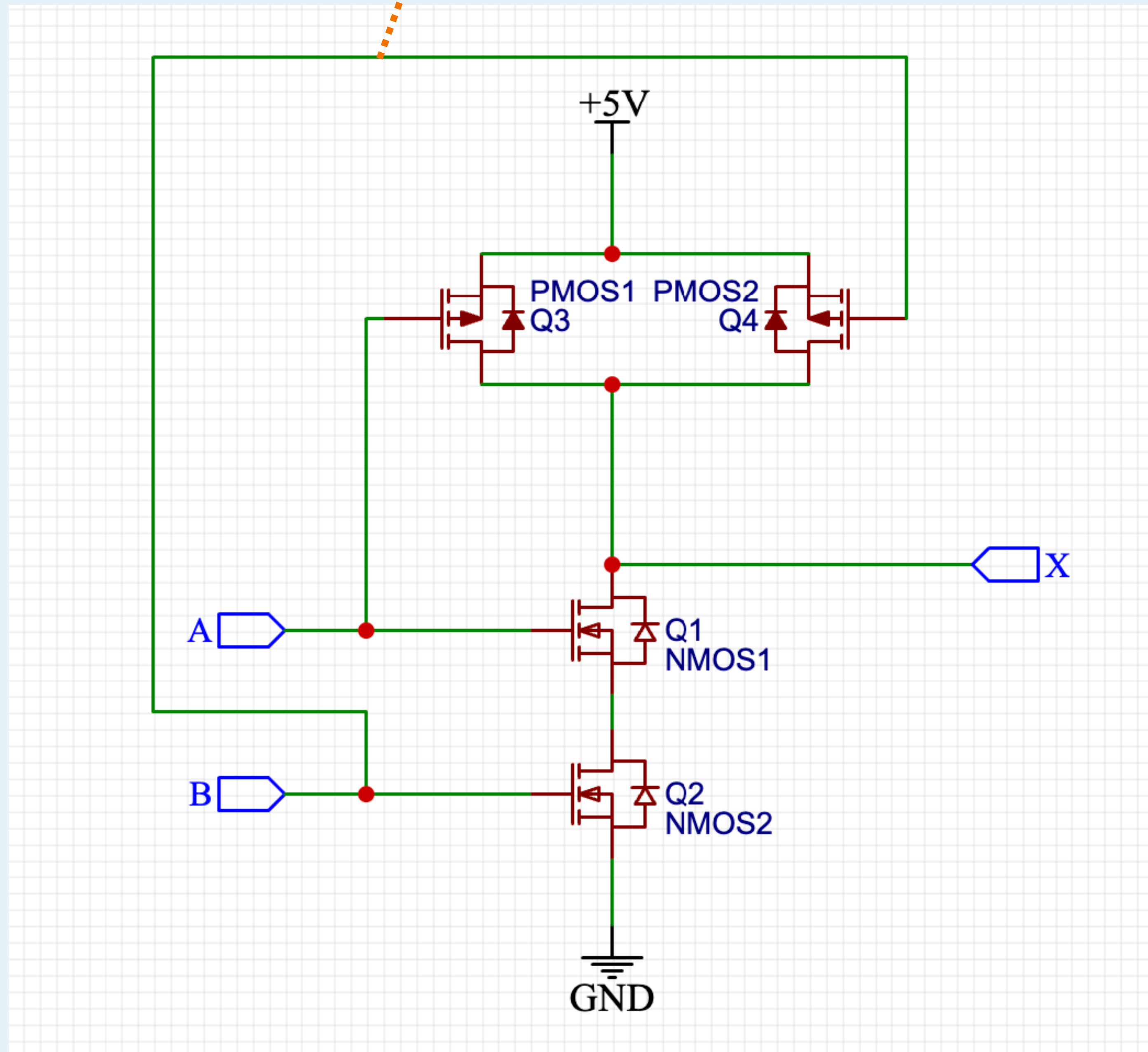


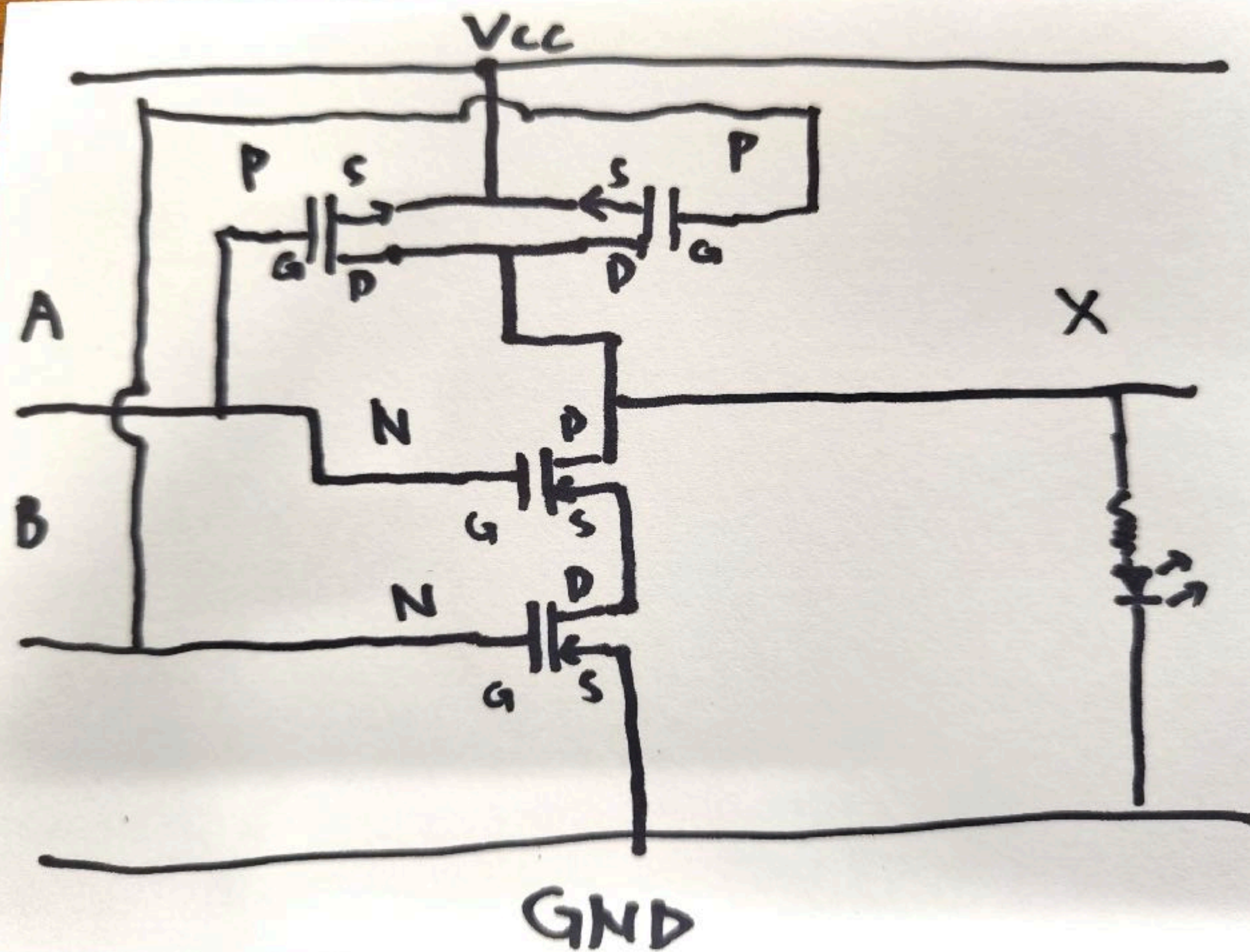

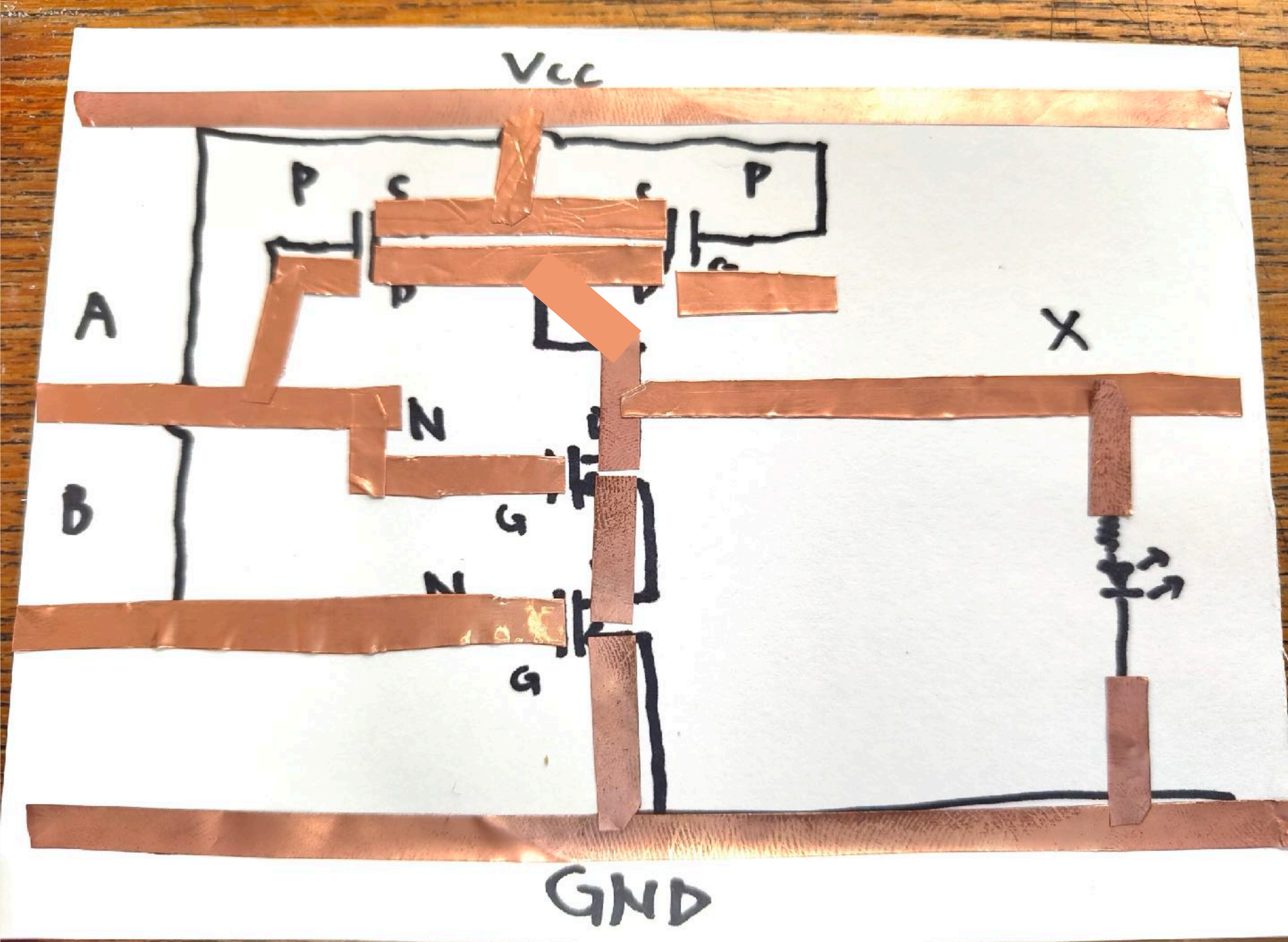


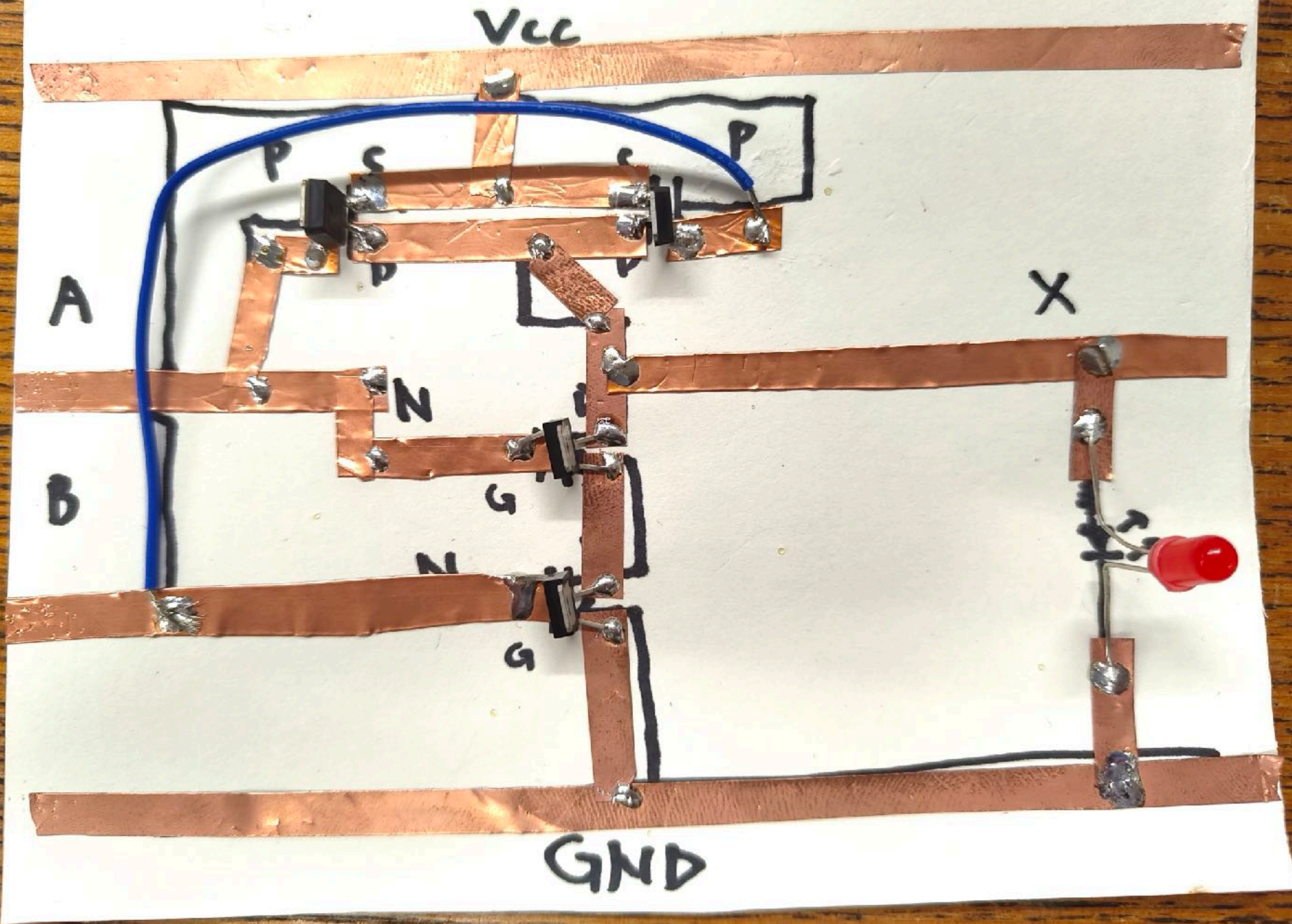


N型
2SK4017

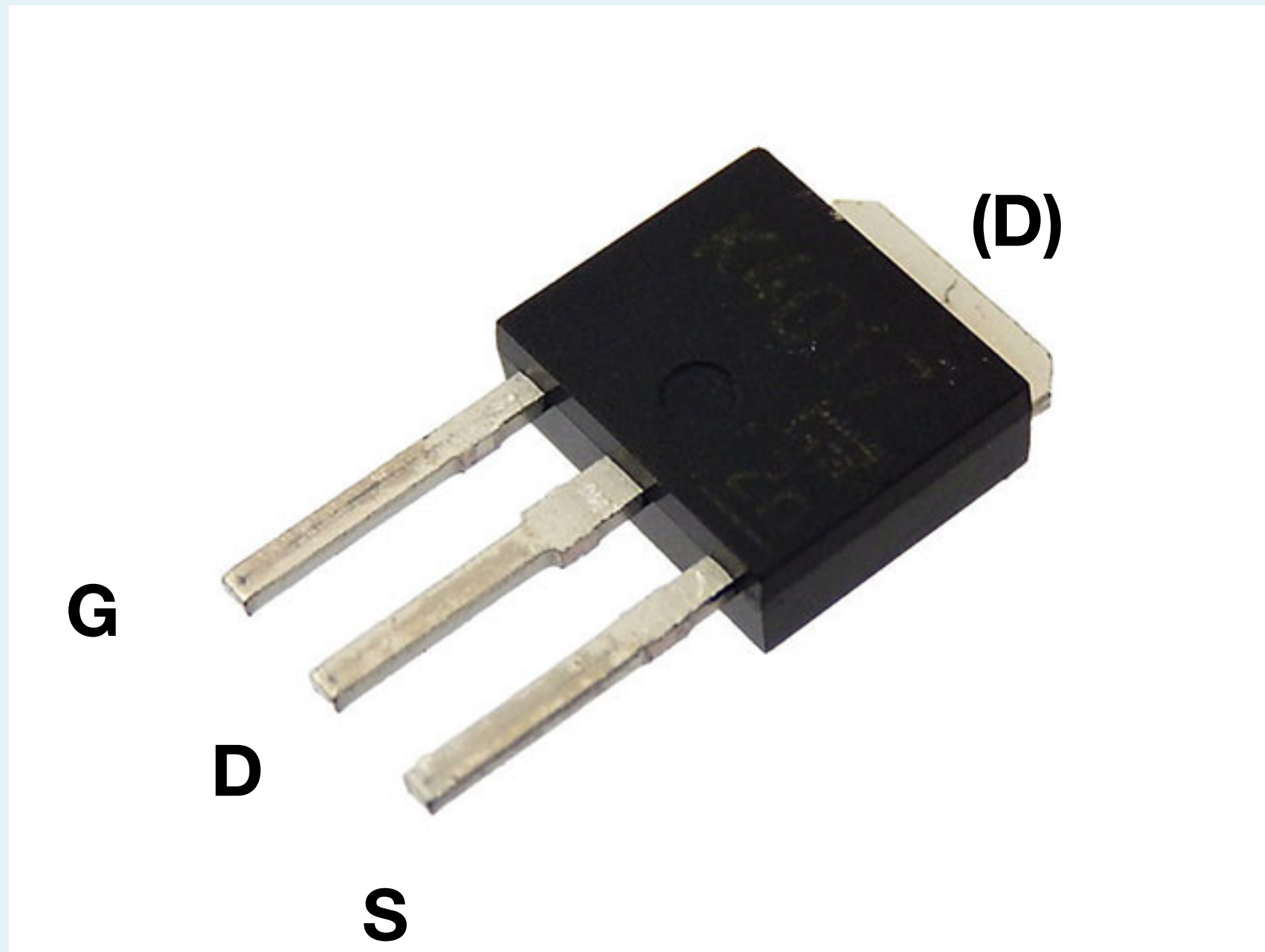


P型
MTP4835
(足が短い)

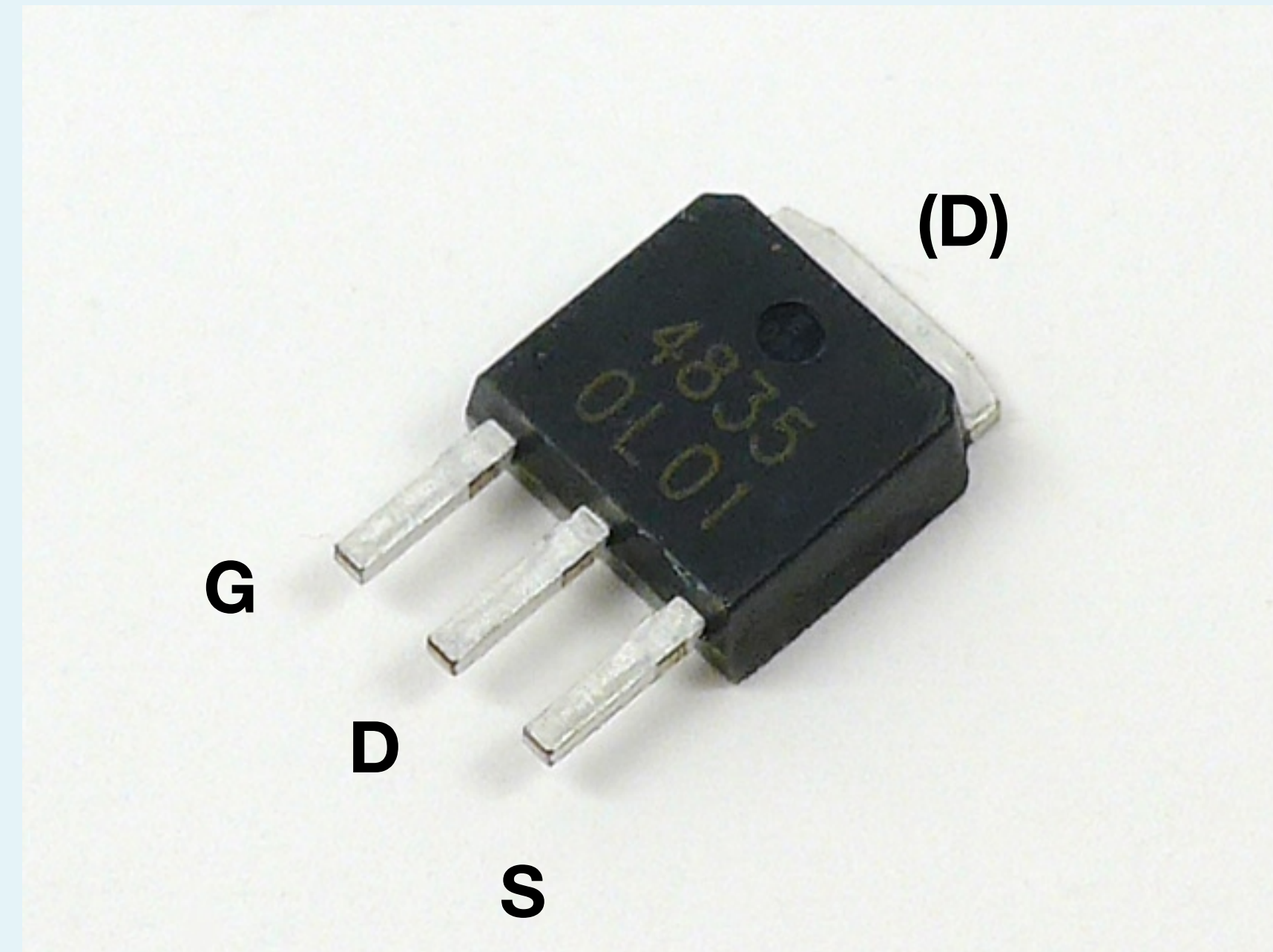


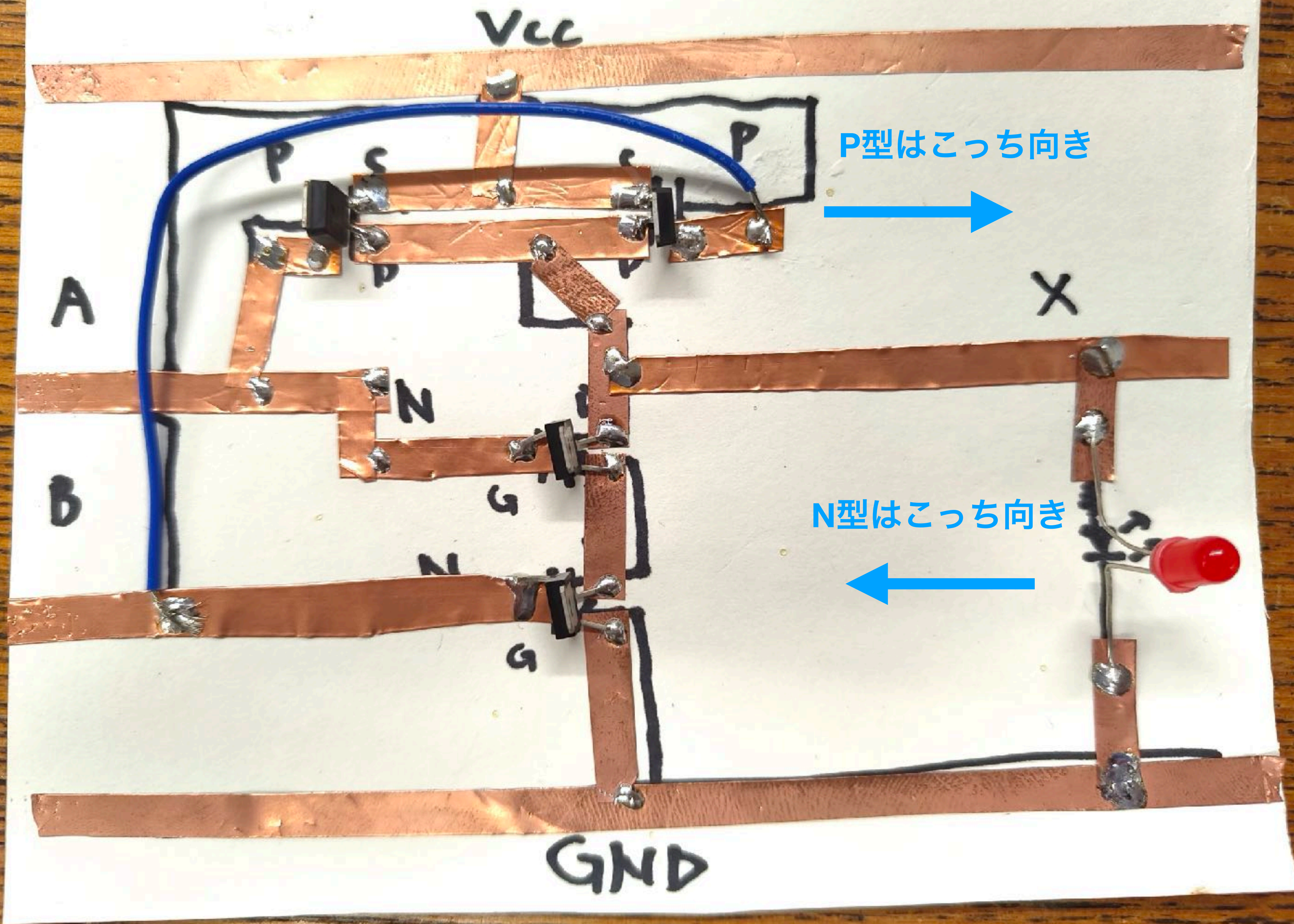


P型はこっち向き

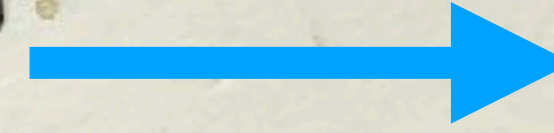


N型はこっち向き

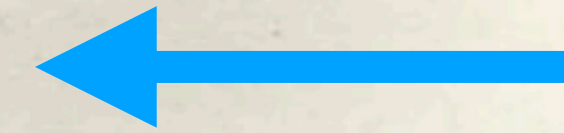


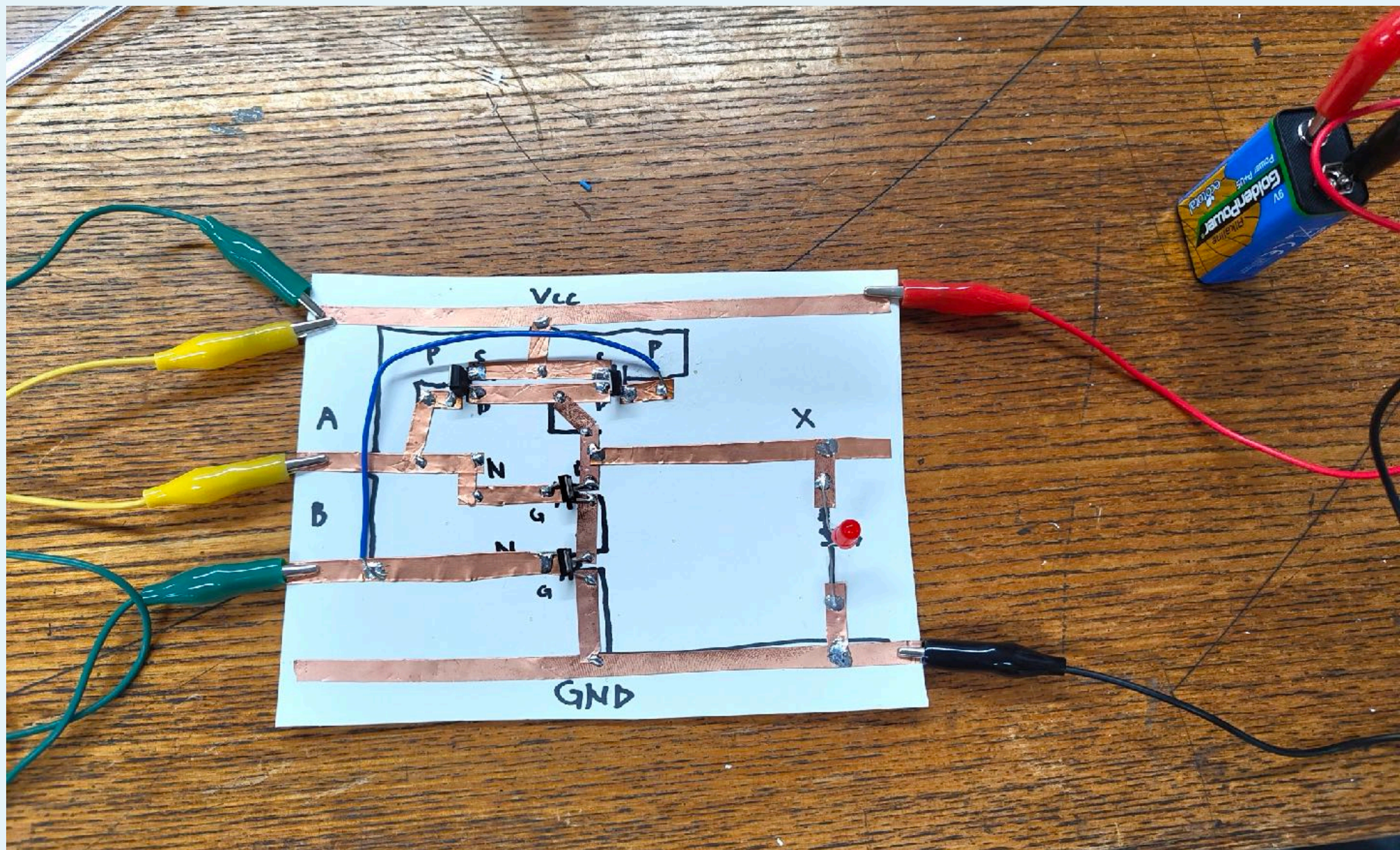


両方入力HIGH：出力LOW

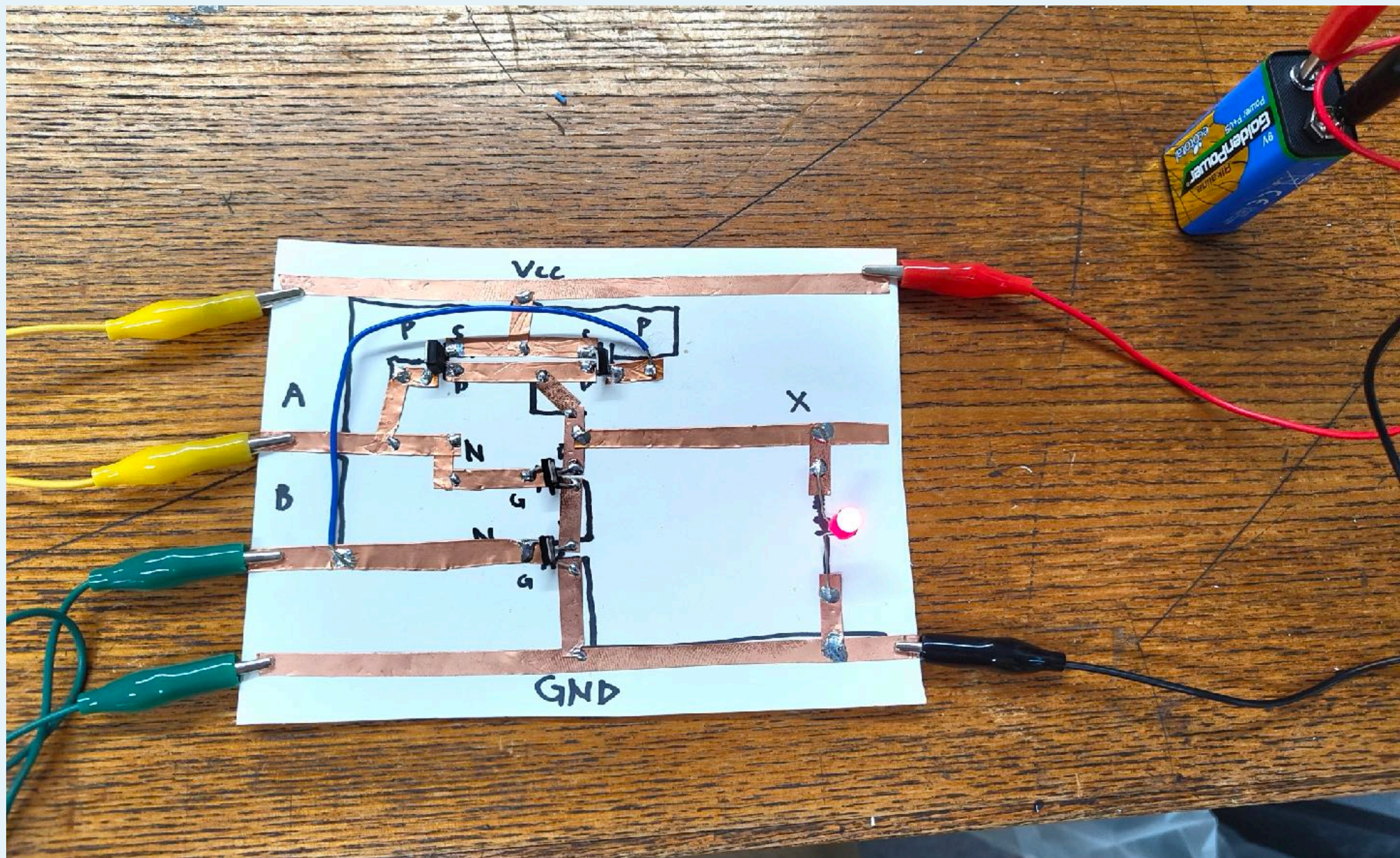

ほかはすべて出力HIGH



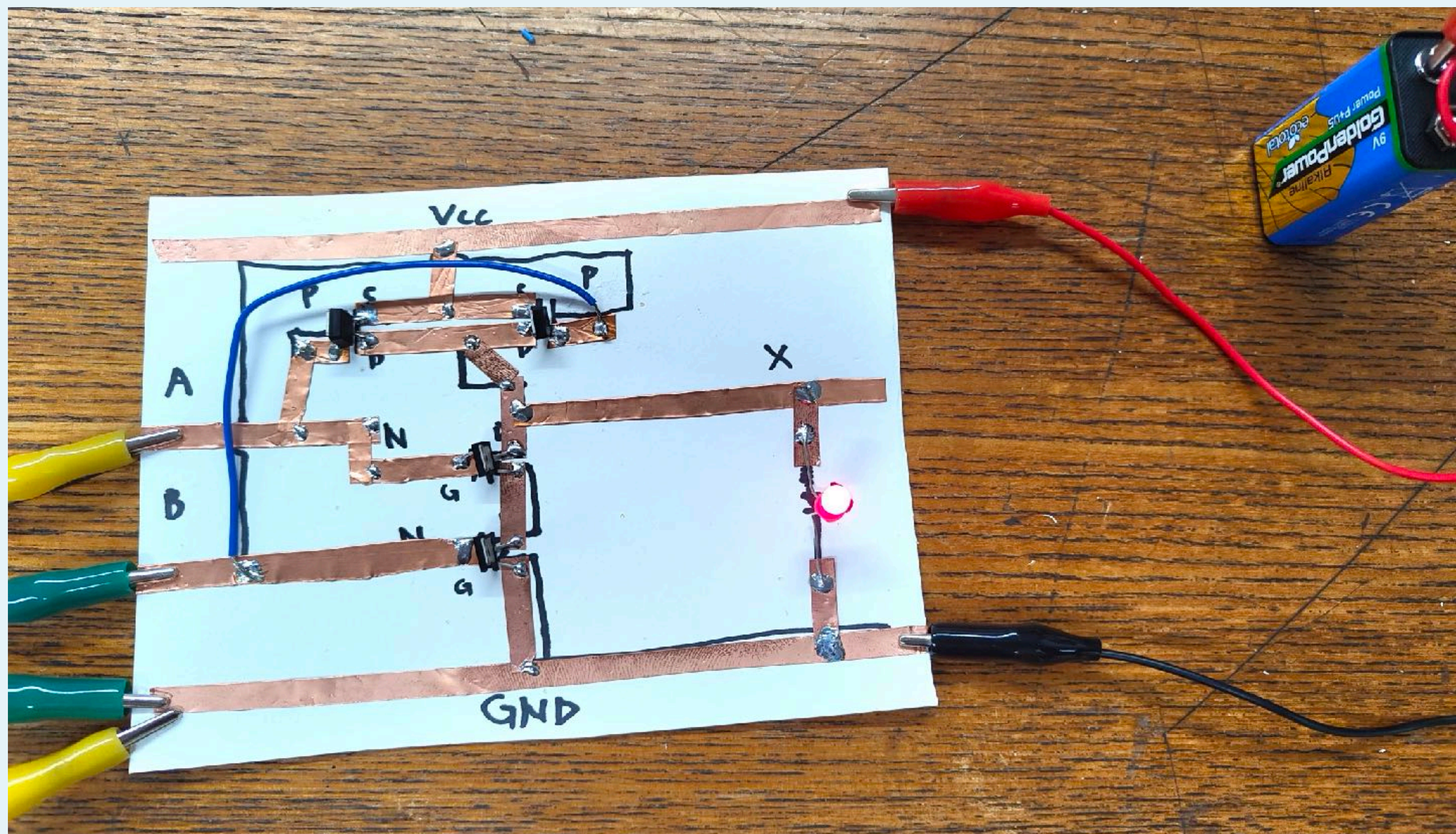


ほかはすべて出力HIGH

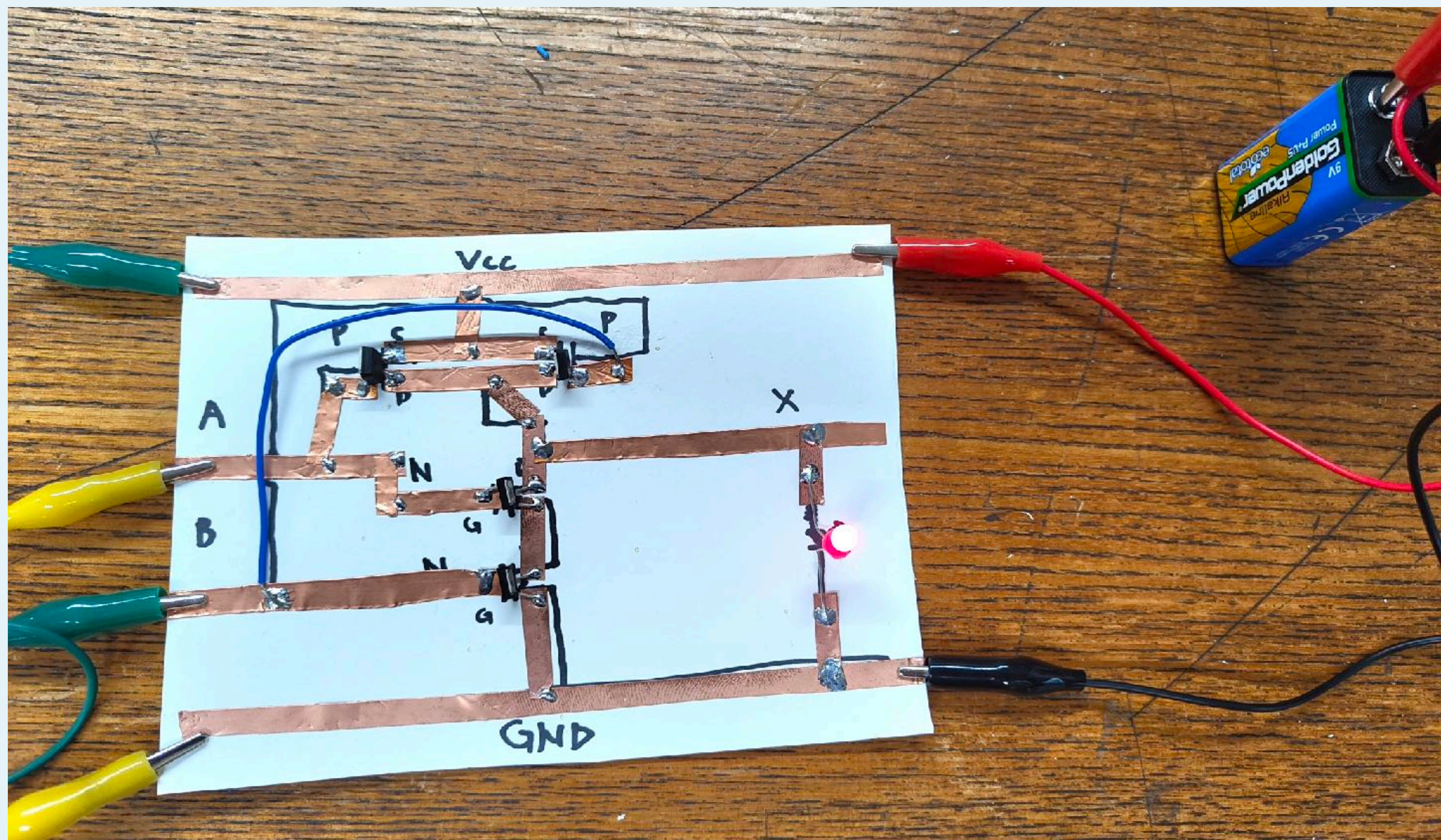

ほかはすべて出力HIGH

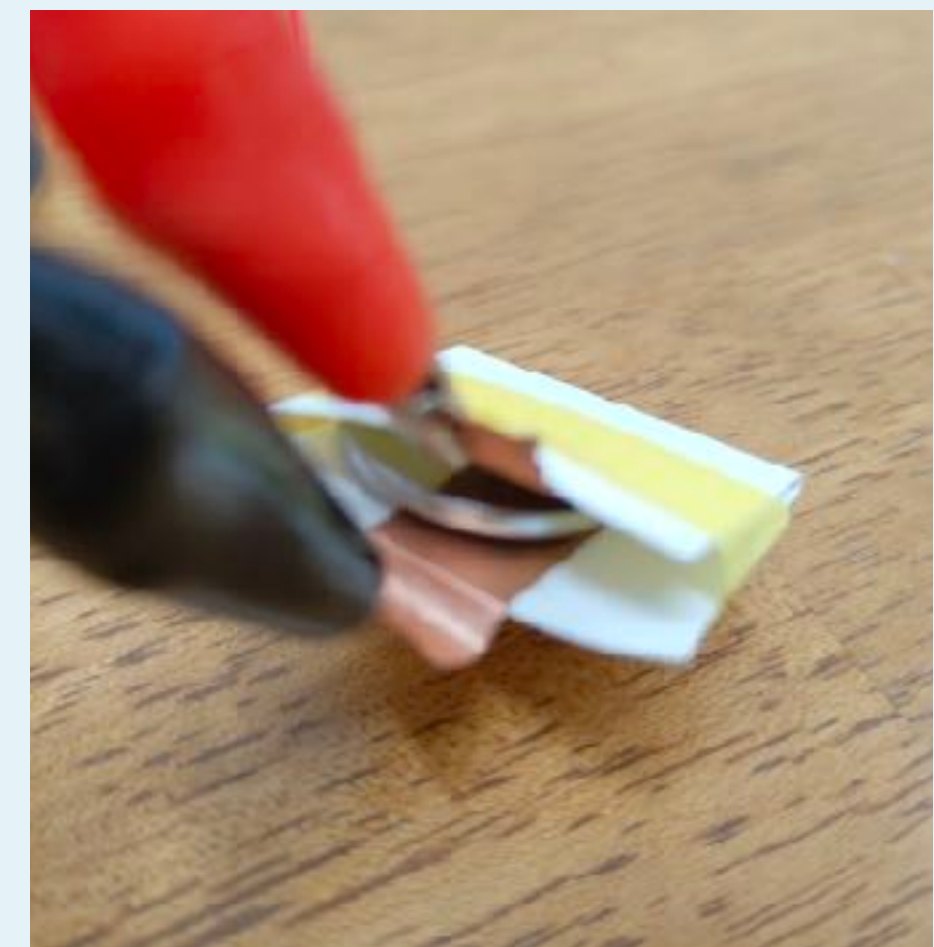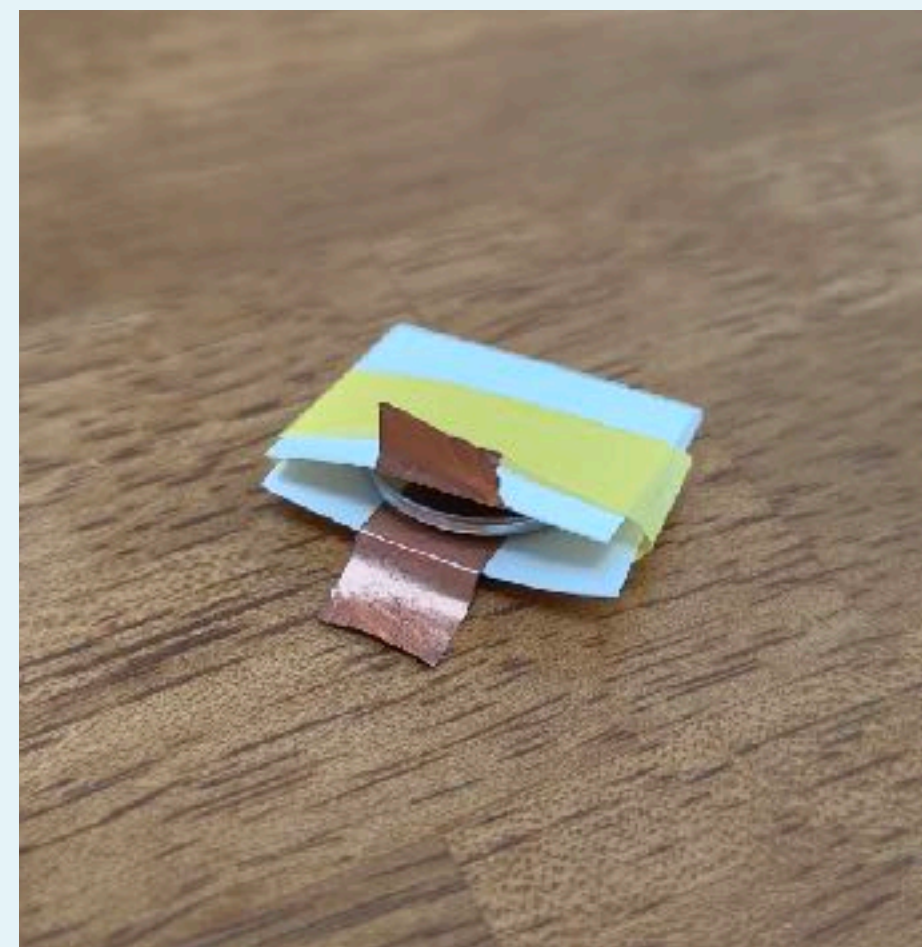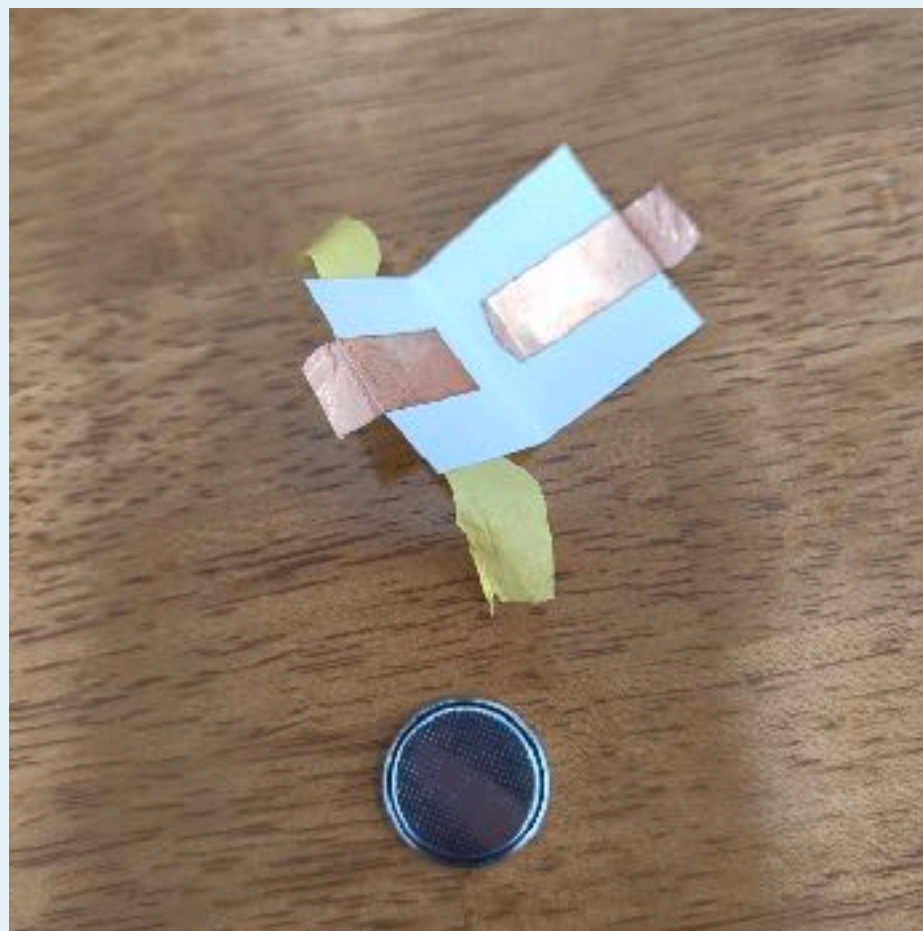- 9V電池でやる場合、FETの向きを間違えるとFETを通してショートして、過熱する可能性があるので、注意
- NAND単体のテストはボタン電池を推奨







SFPC Summer in Yamaguchi 2019 での製作例(左：大網拓真、右：Chara Wang)



https://makezine.jp/blog/2019/11/sfpc_report_01.html

NANDゲートから加算器を作るう





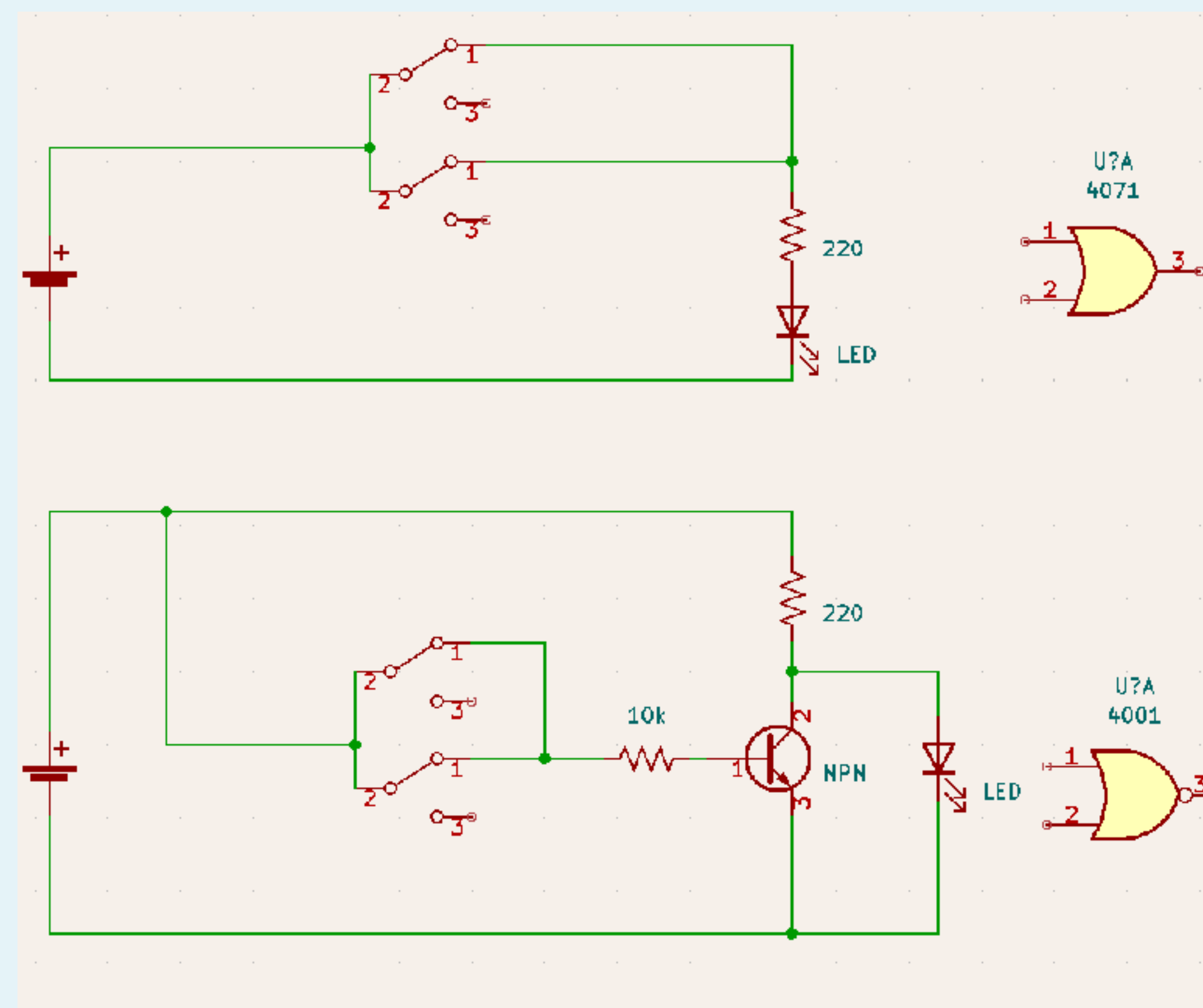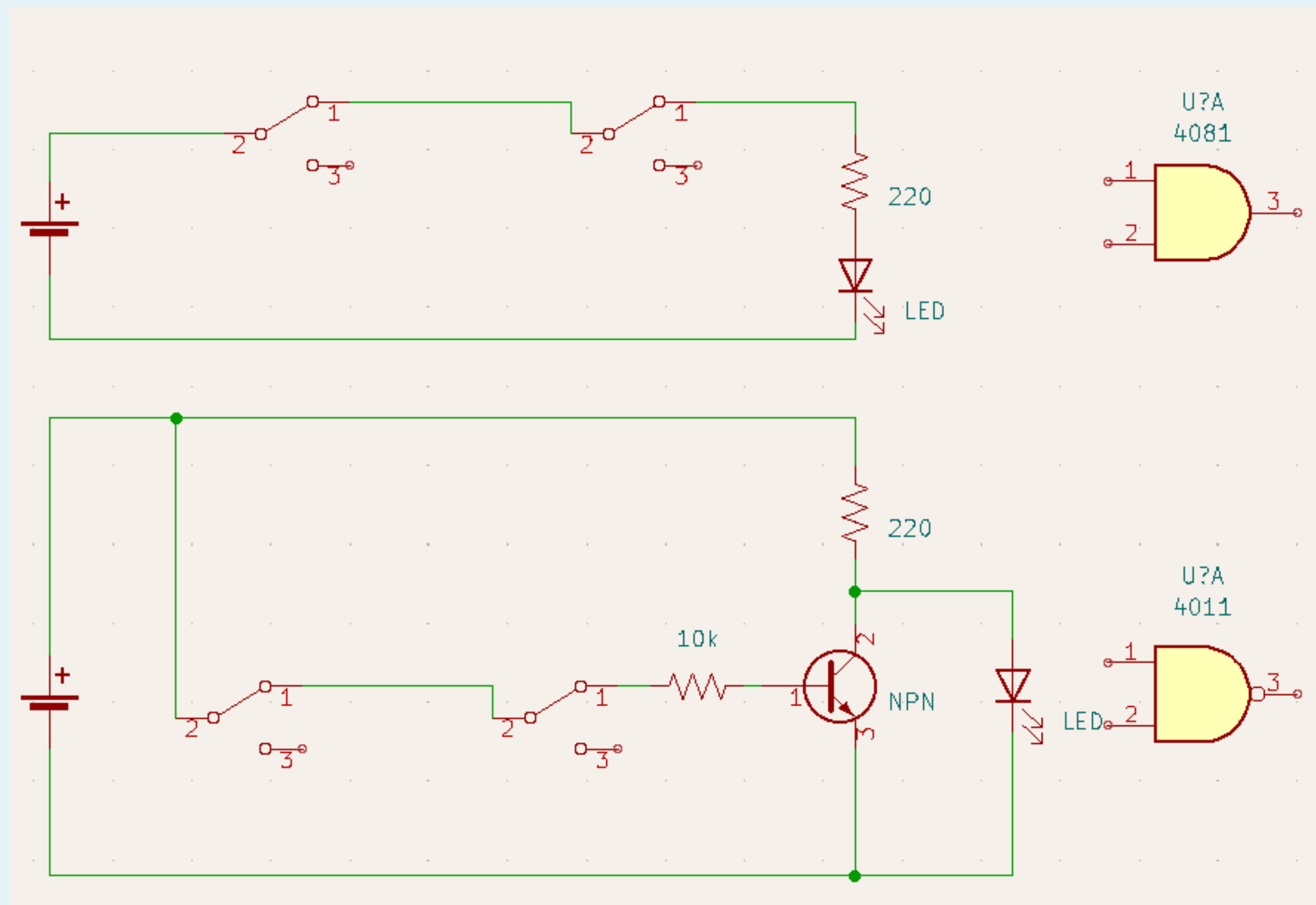



AND

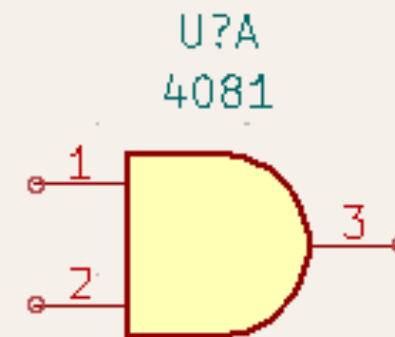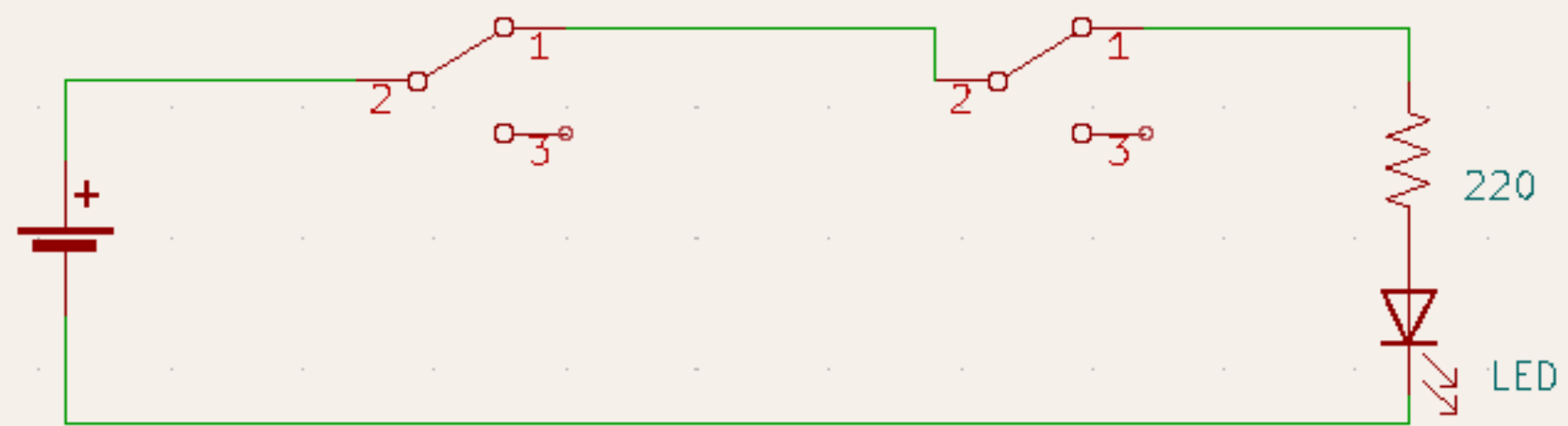



NAND

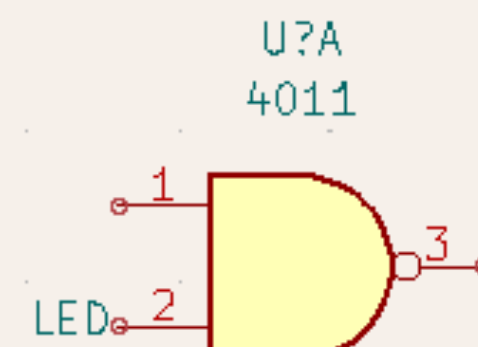
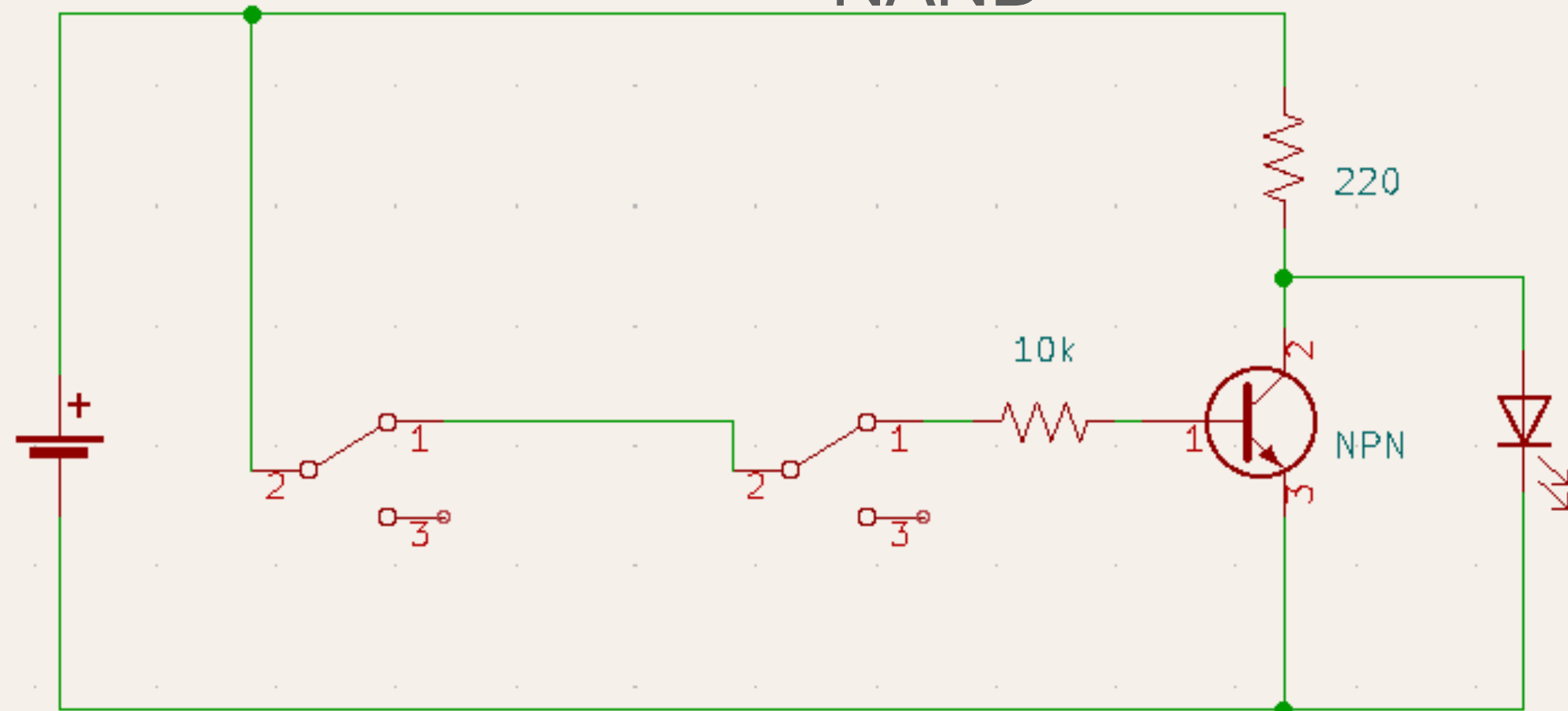


OR

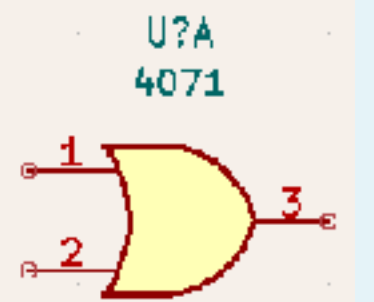
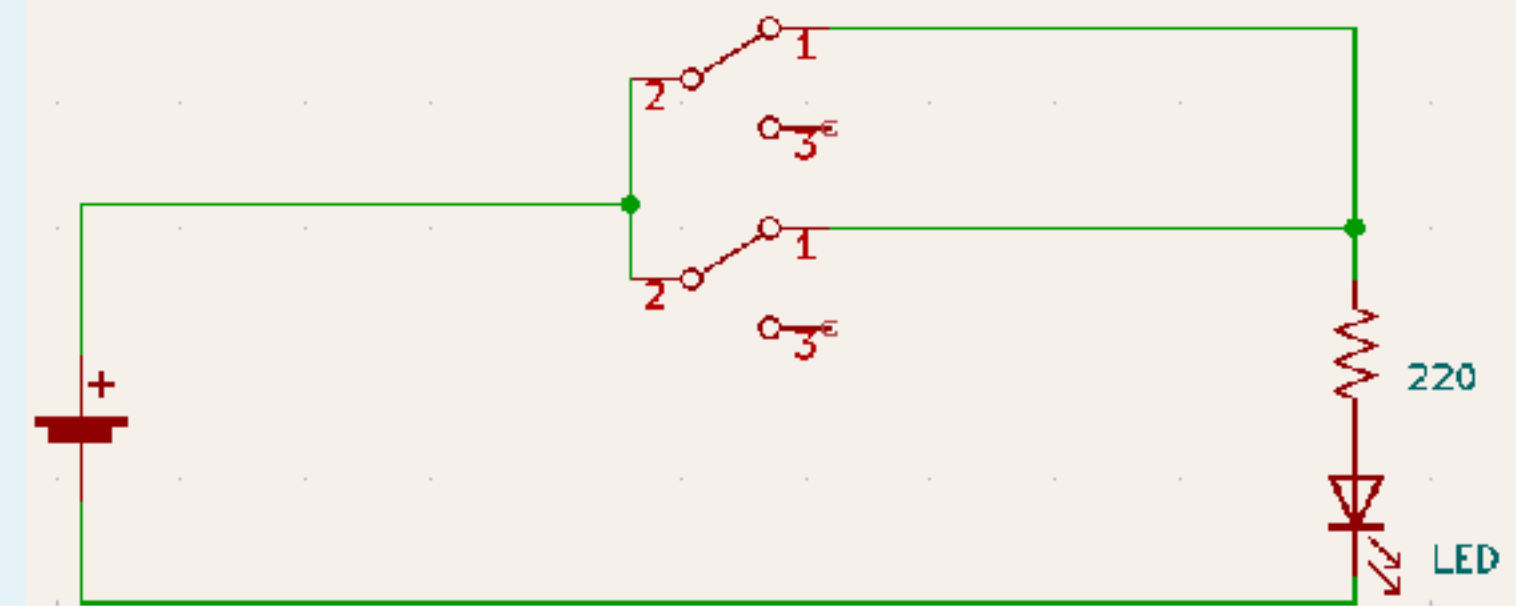


NOR

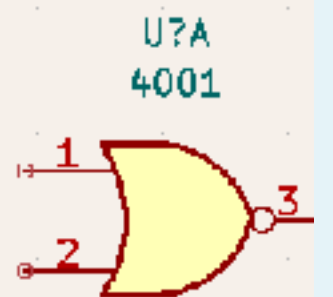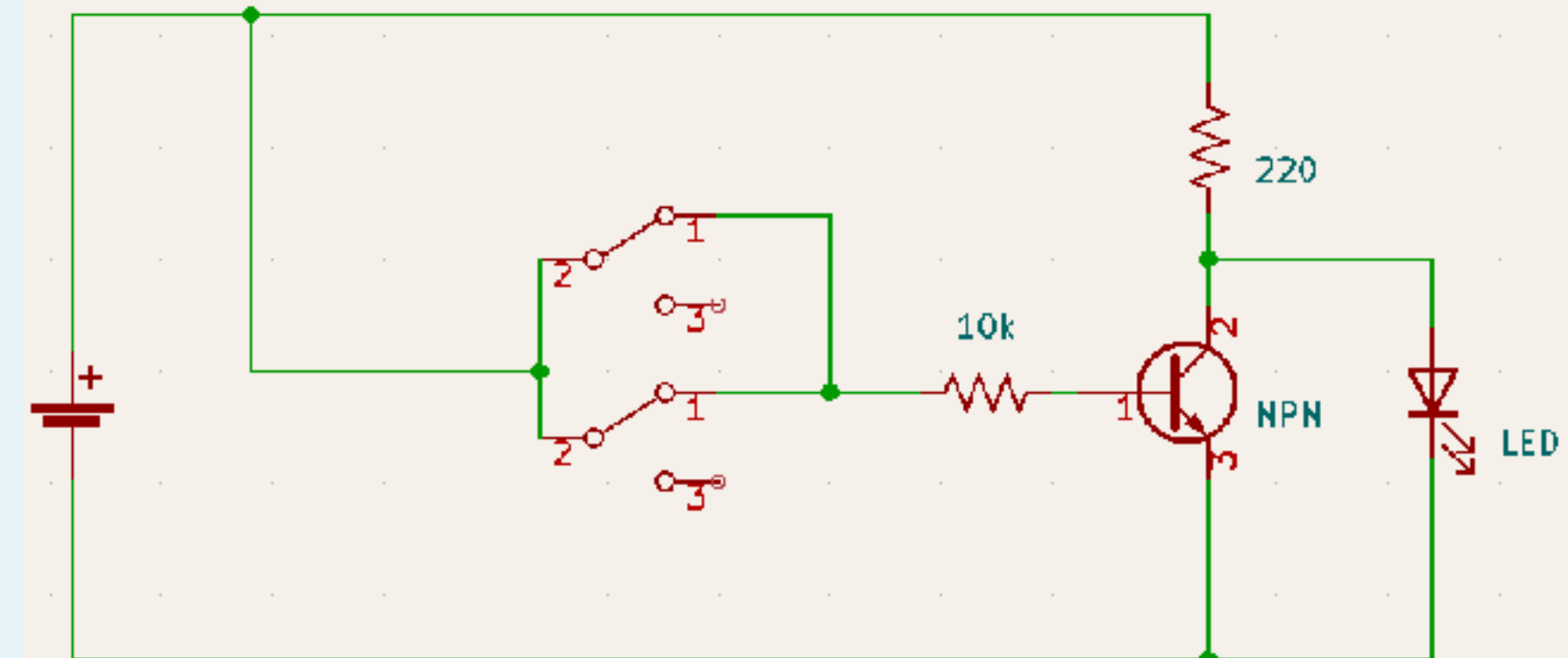


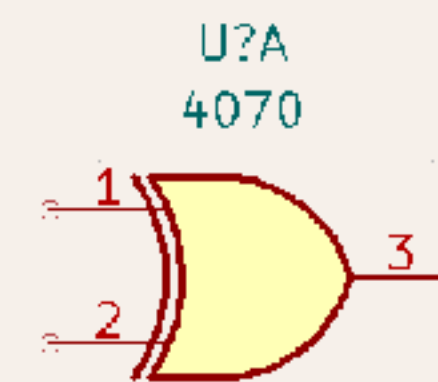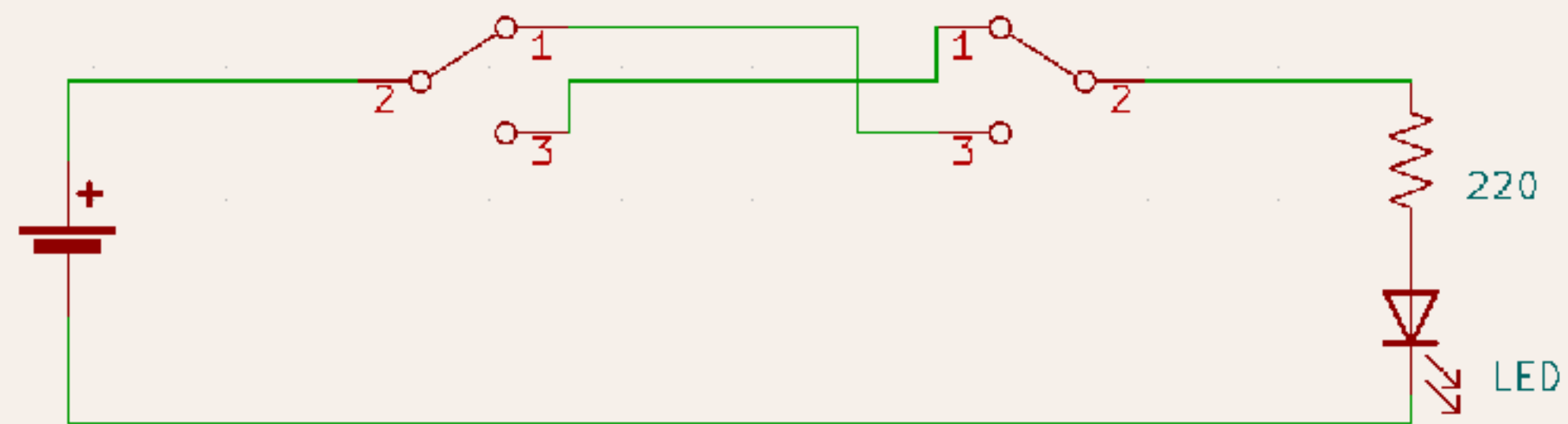


XOR

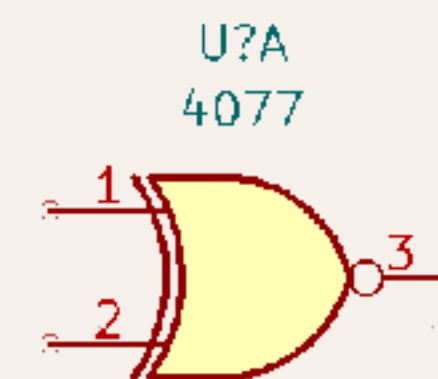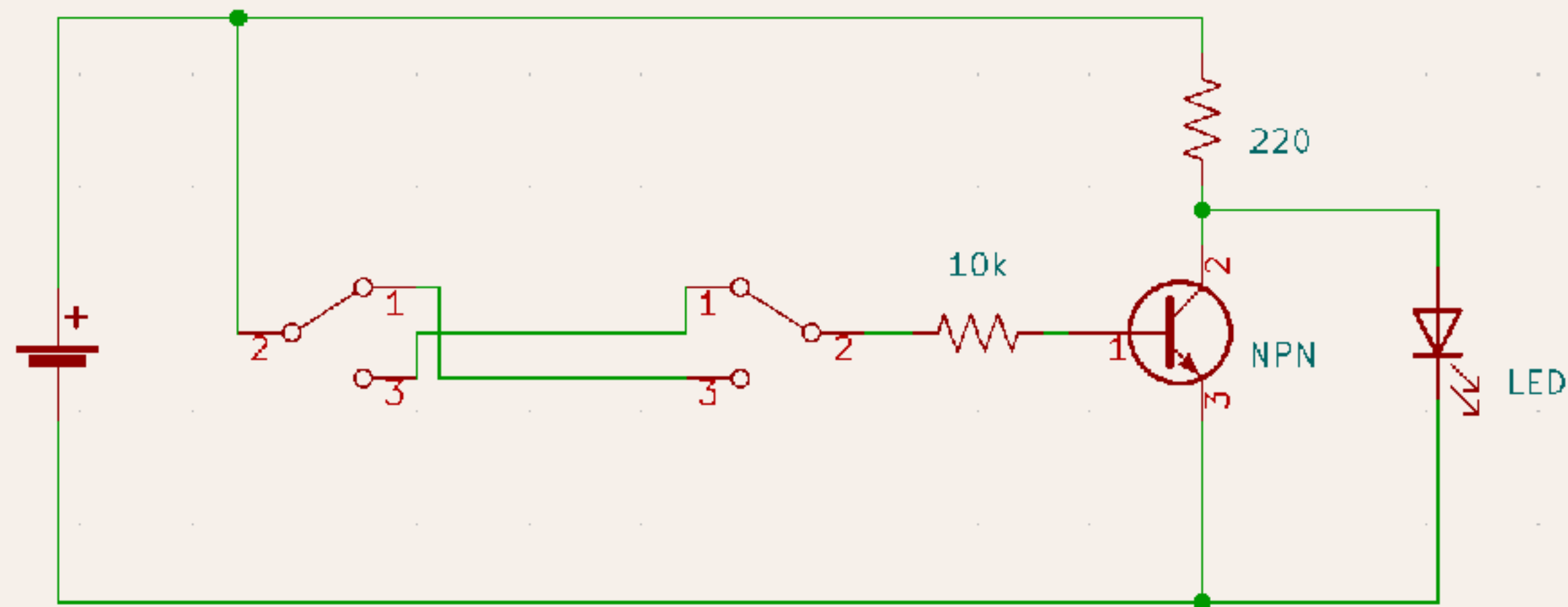


XNOR

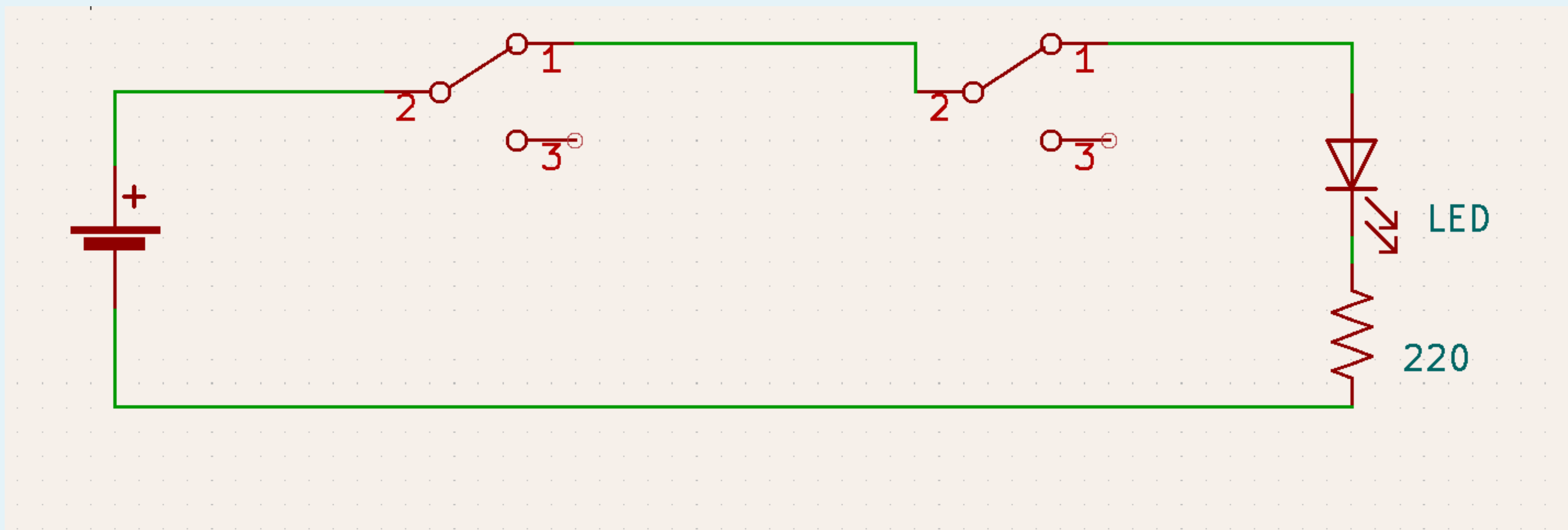

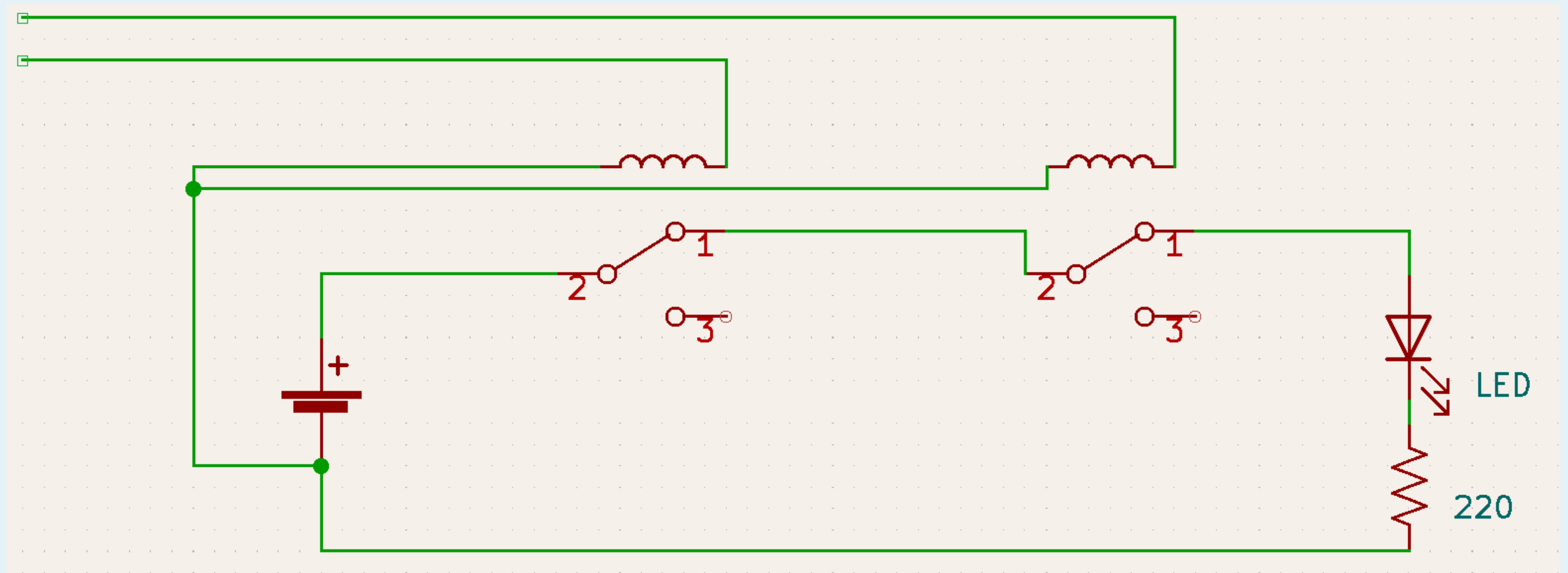


スイッチのオンオフも、電氣的にコントロールしたい

NANDからNOT

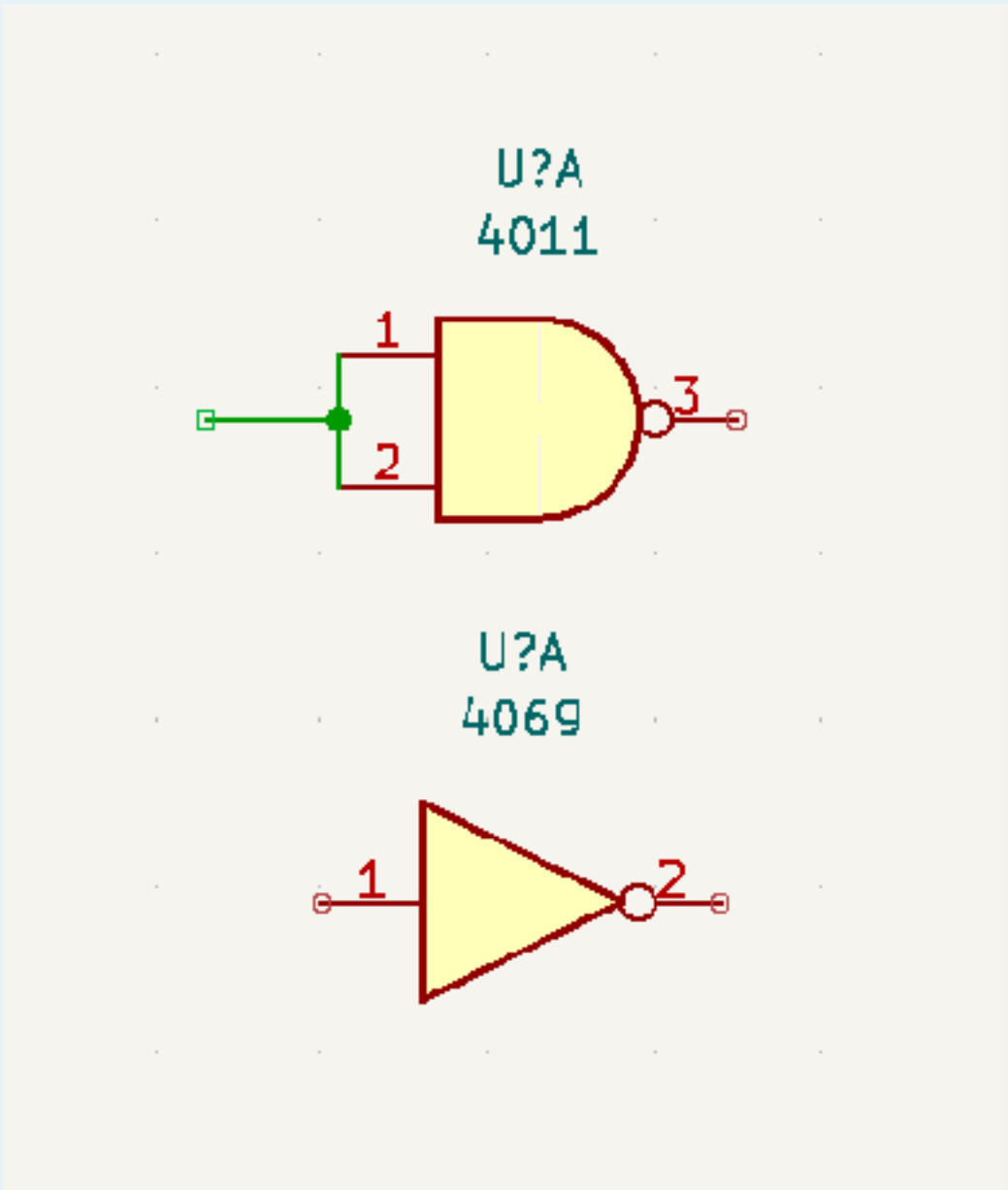


A	B	X
0	0	1
0	1	1
1	0	1
1	1	0

NANDからNOT

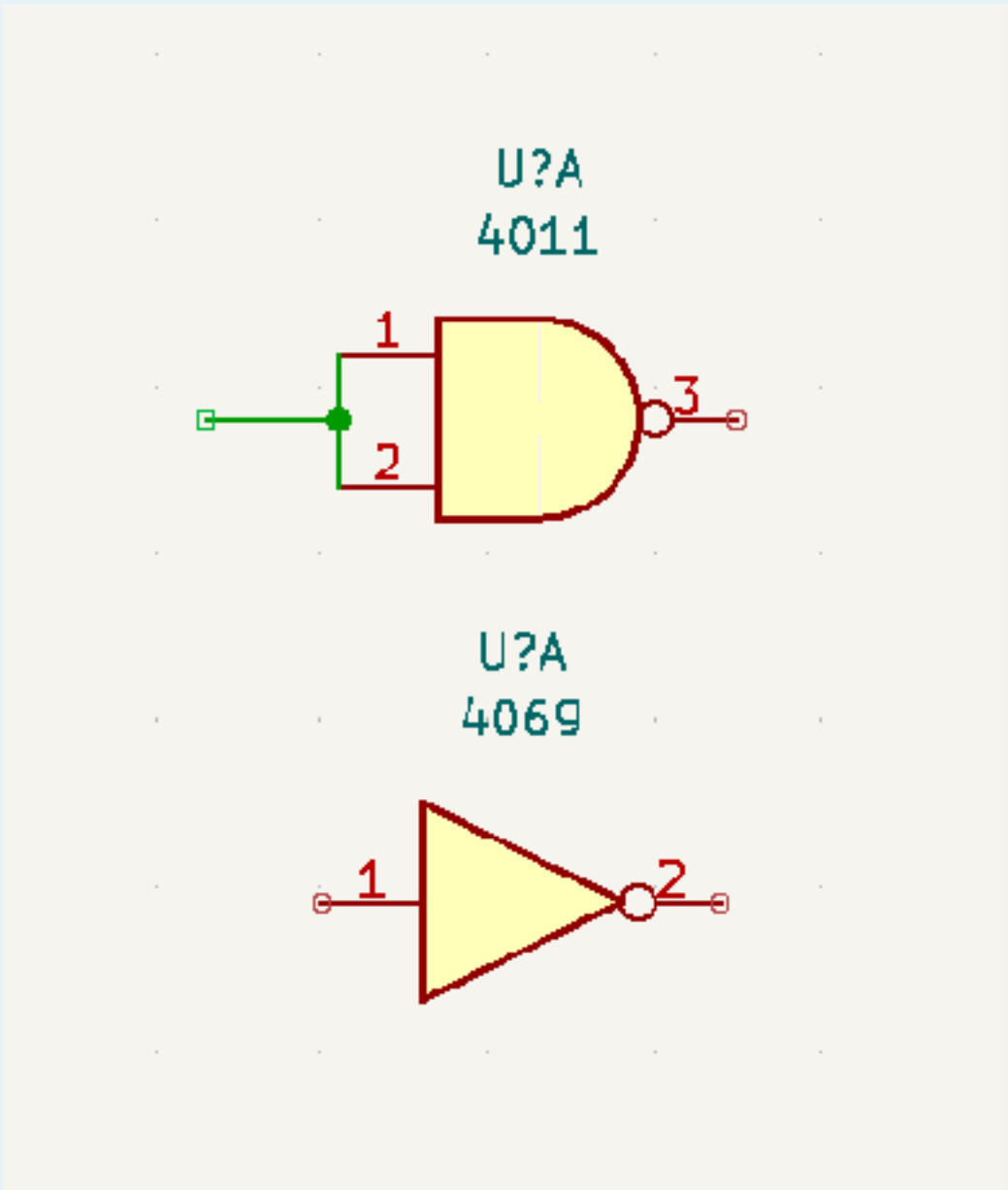


A	B	X
0	0	1
0	1	1
1	0	1
1	1	0

NANDからAND

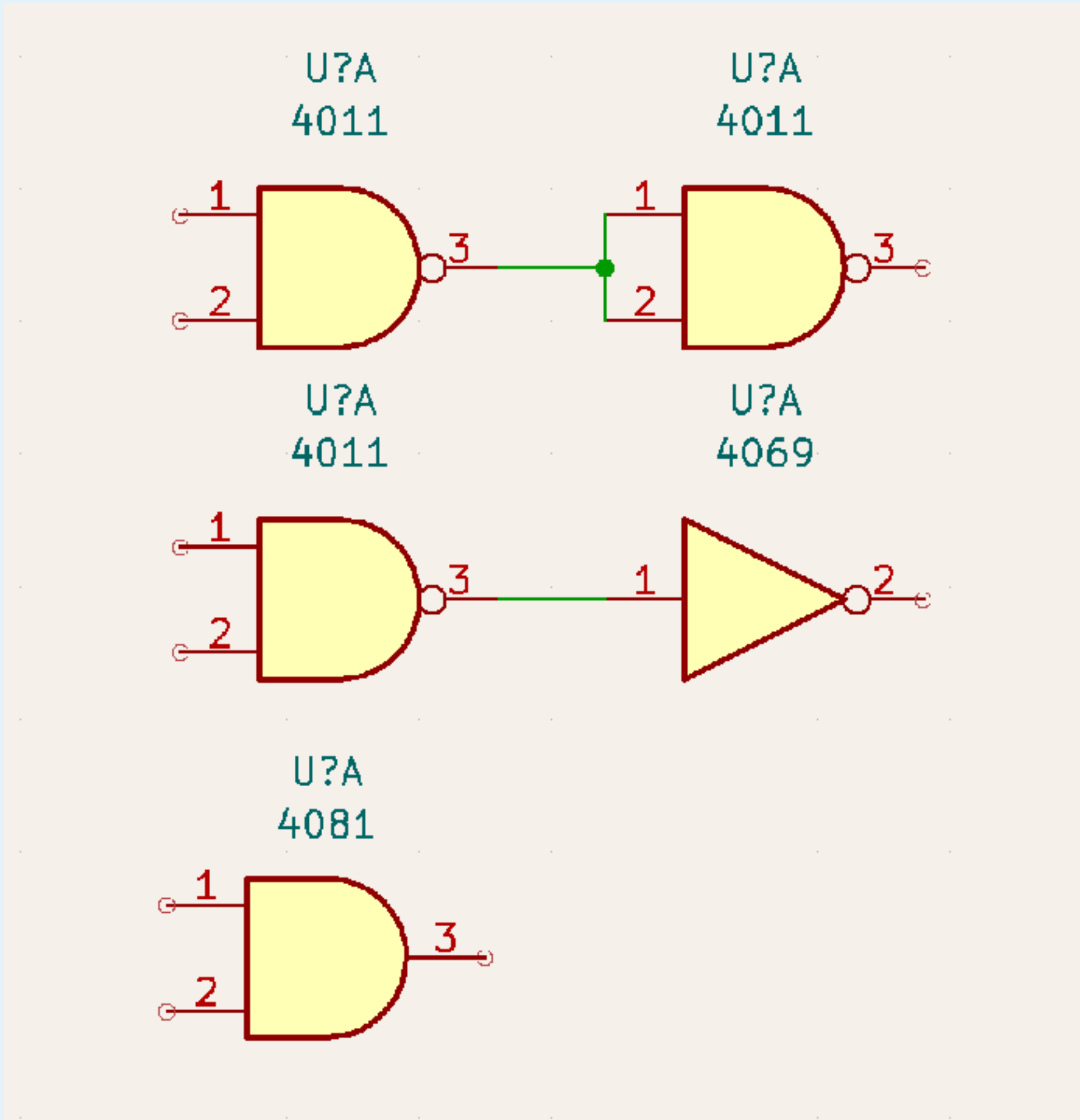


A	B	X	NOT(X)
0	0	1	0
0	1	1	0
1	0	1	0
1	1	0	1

NANDからOR

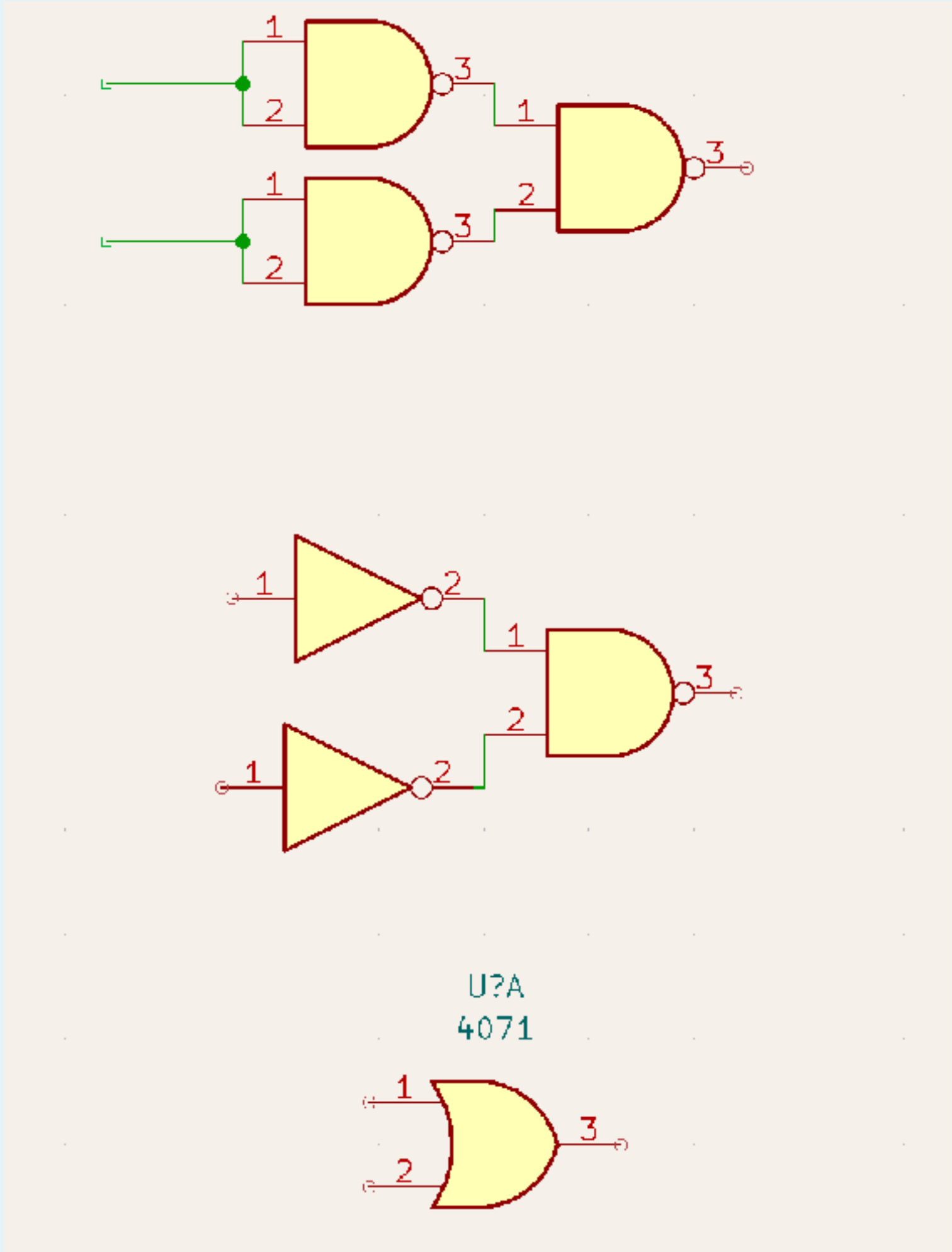


A	NOT(A)	B	NOT(B)	OR(A,B)
0	1	0	1	0
0	1	1	0	1
1	0	0	1	1
1	0	1	0	1


NANDからXOR

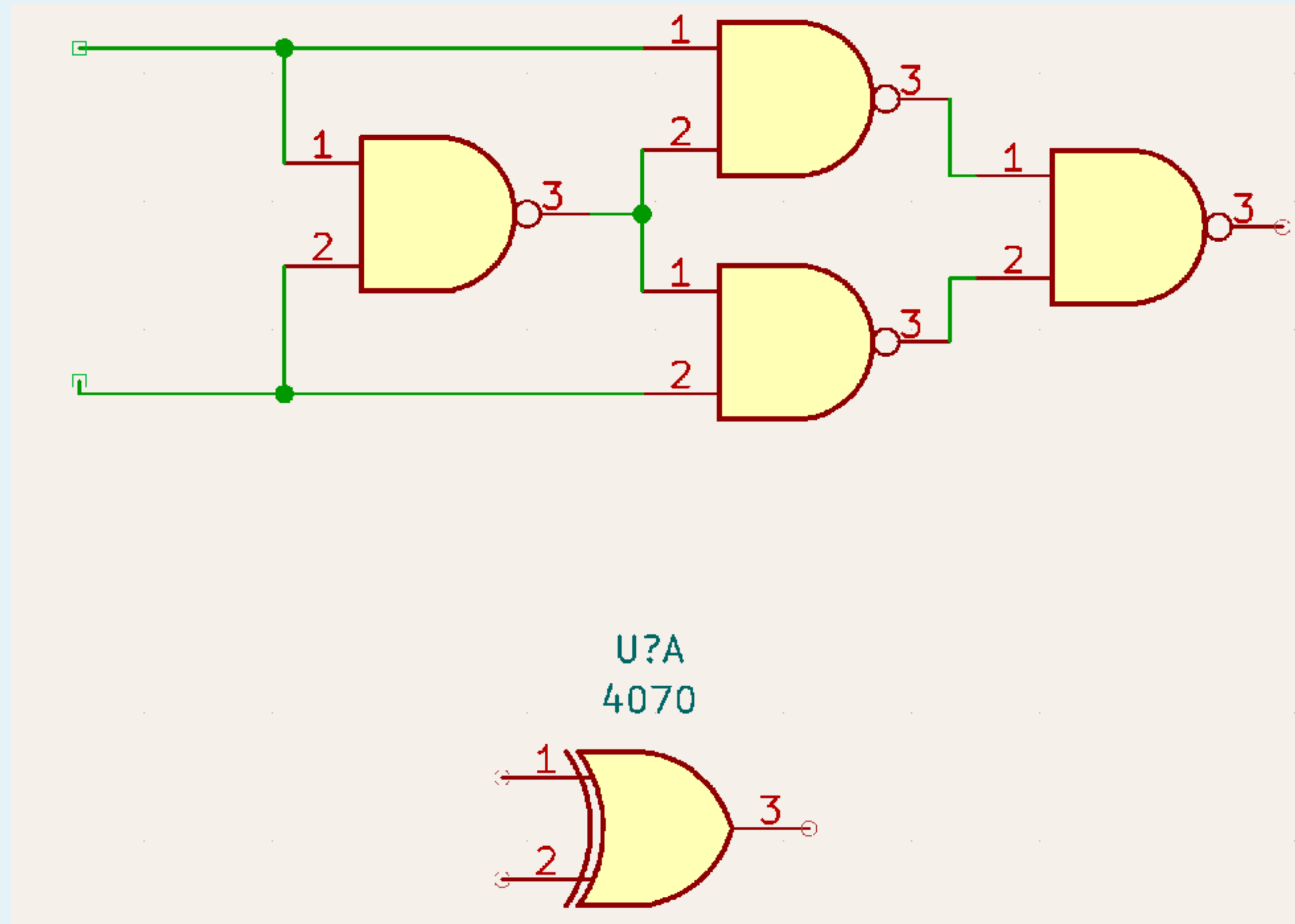


NANDからXOR

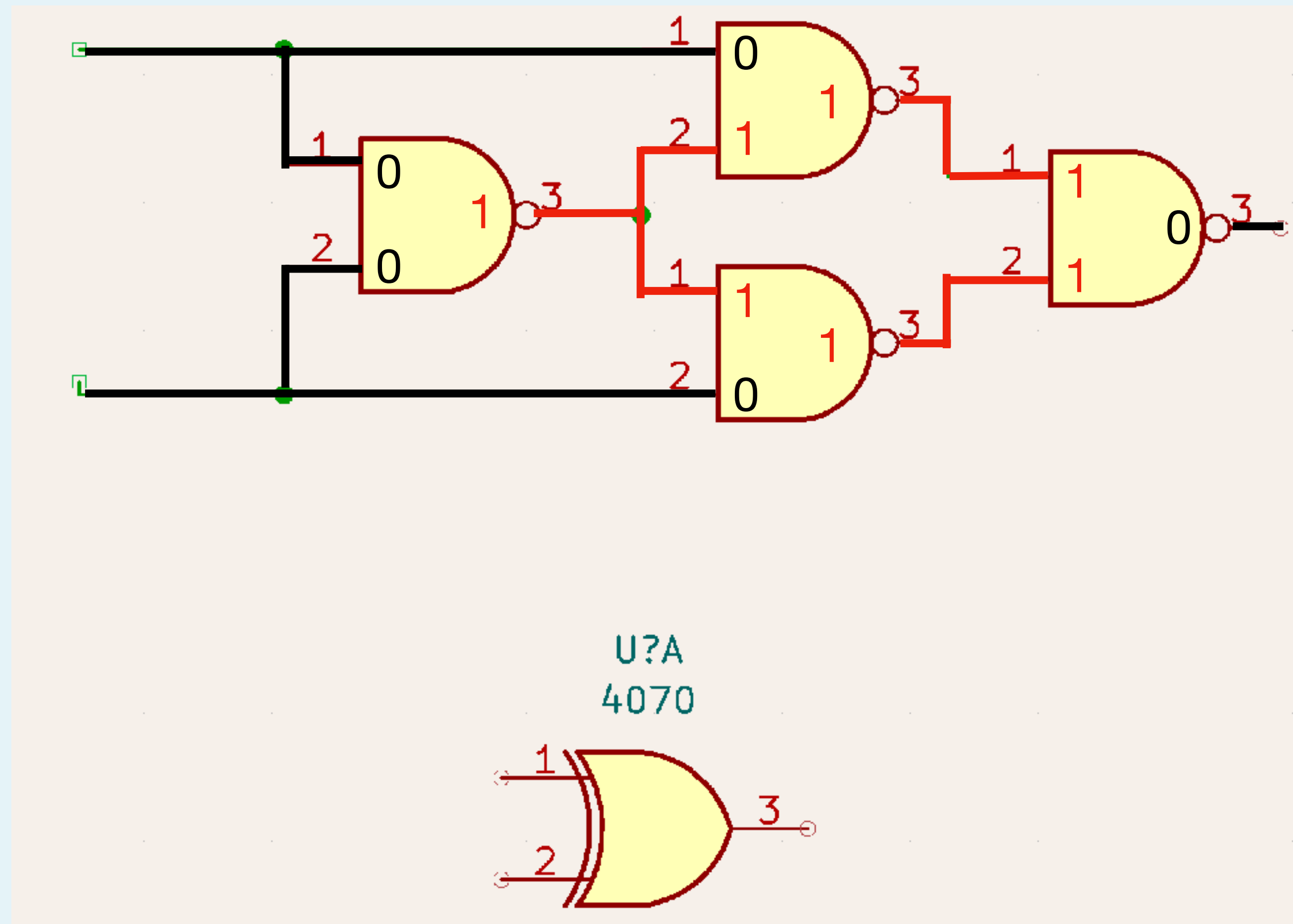


NANDからXOR

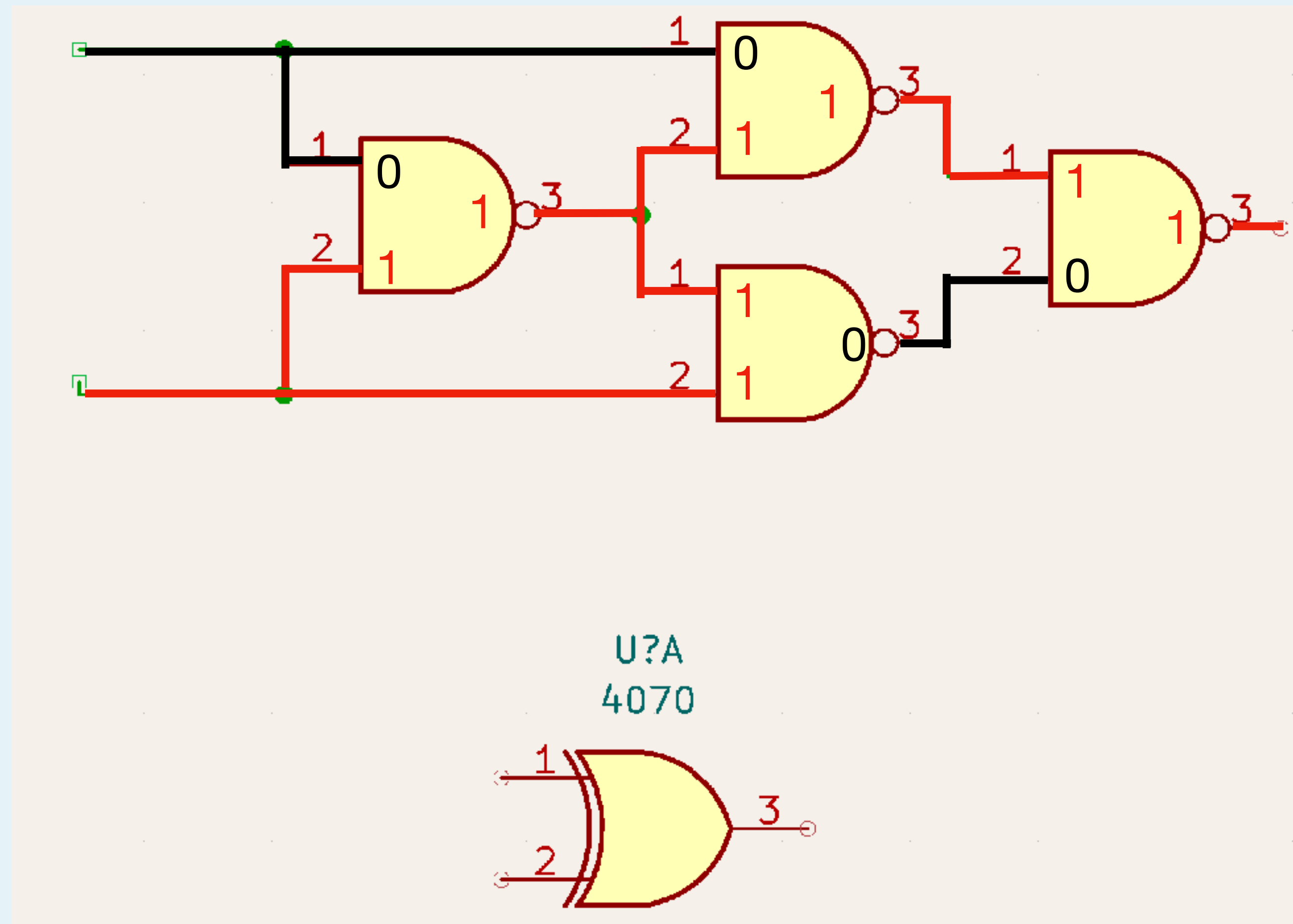

NANDからXOR

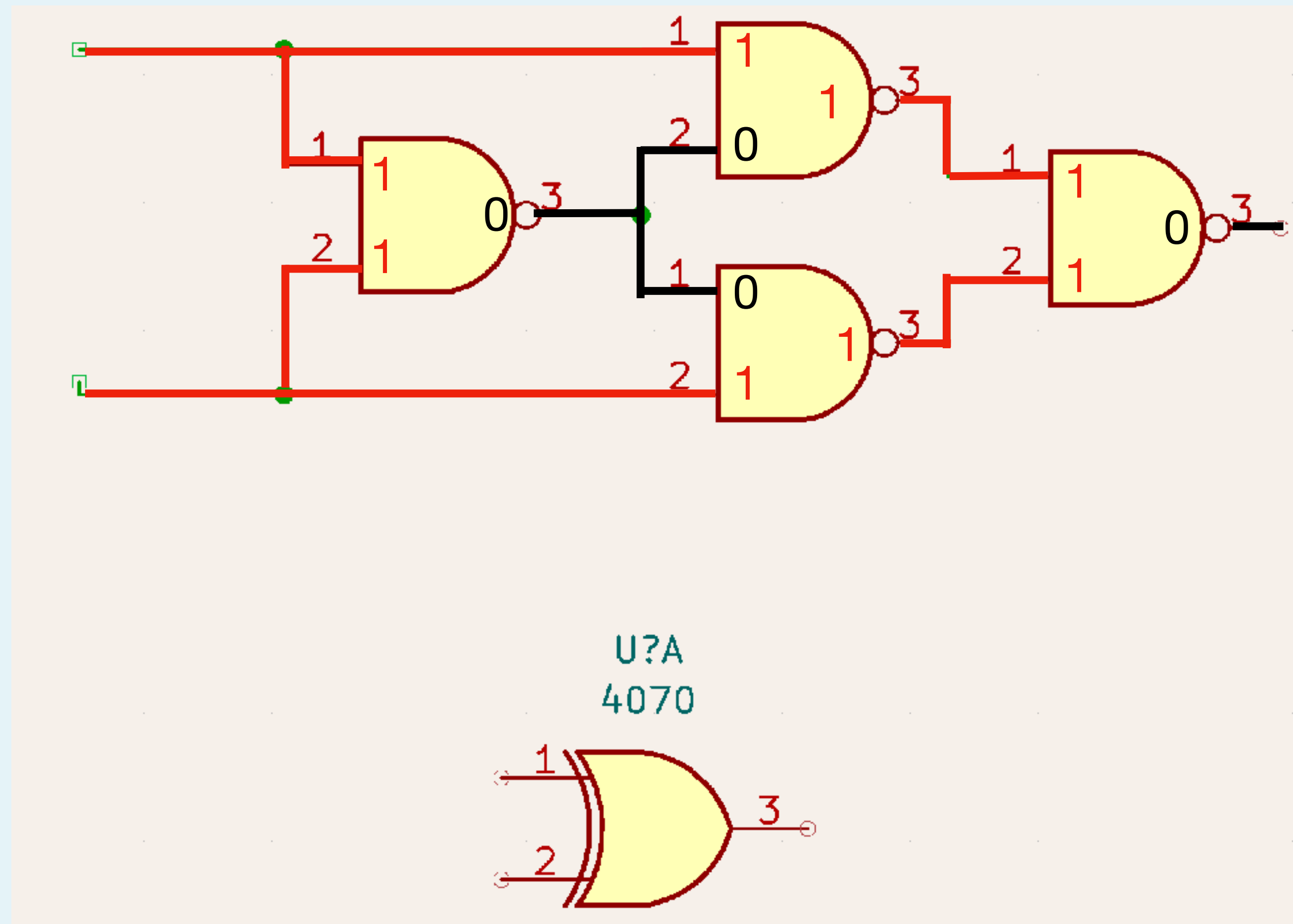


半加算器(一桁入力の足し算)

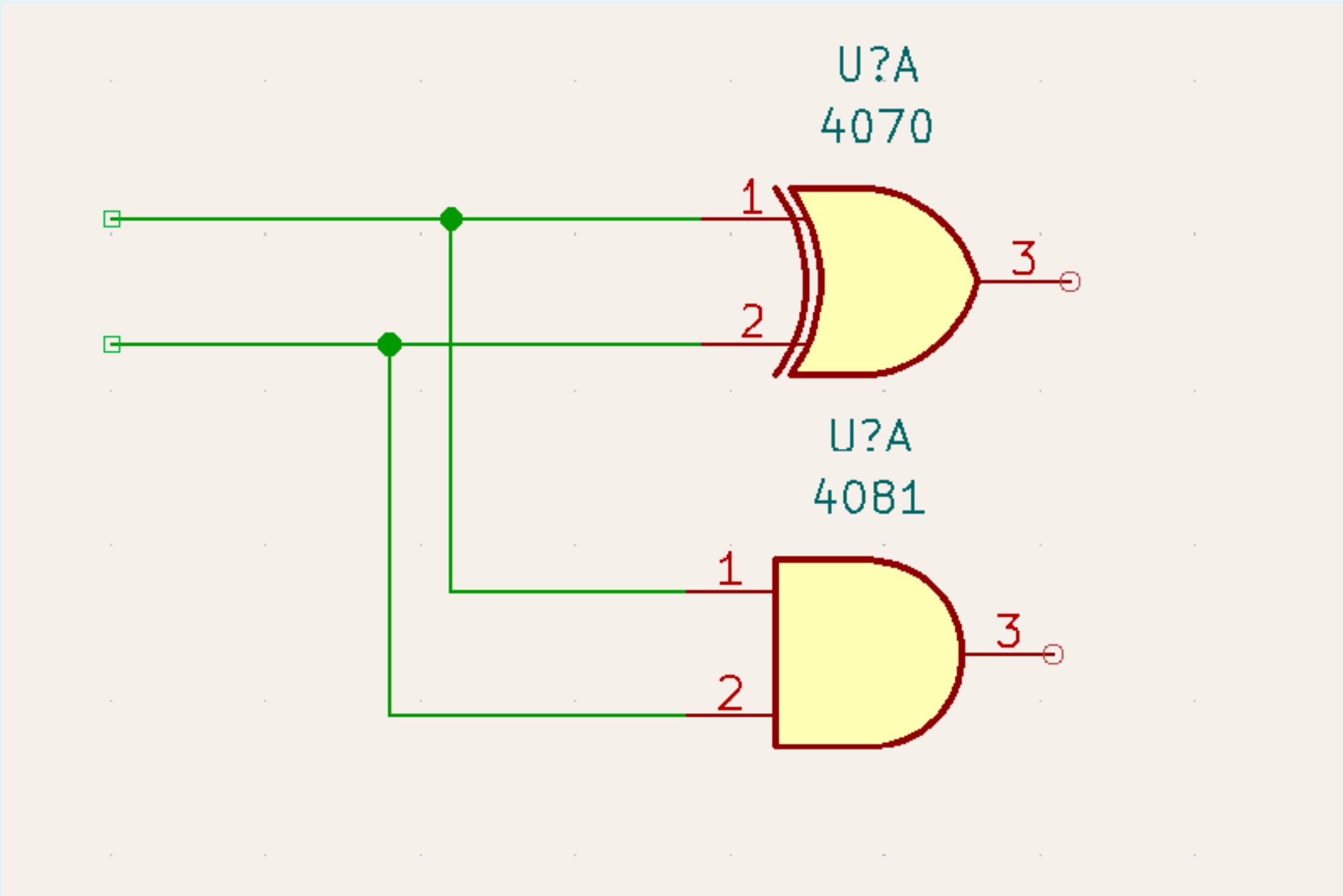


A	B	A+B(上位)	A+B (下位)
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

半加算器(一桁入力の足し算)

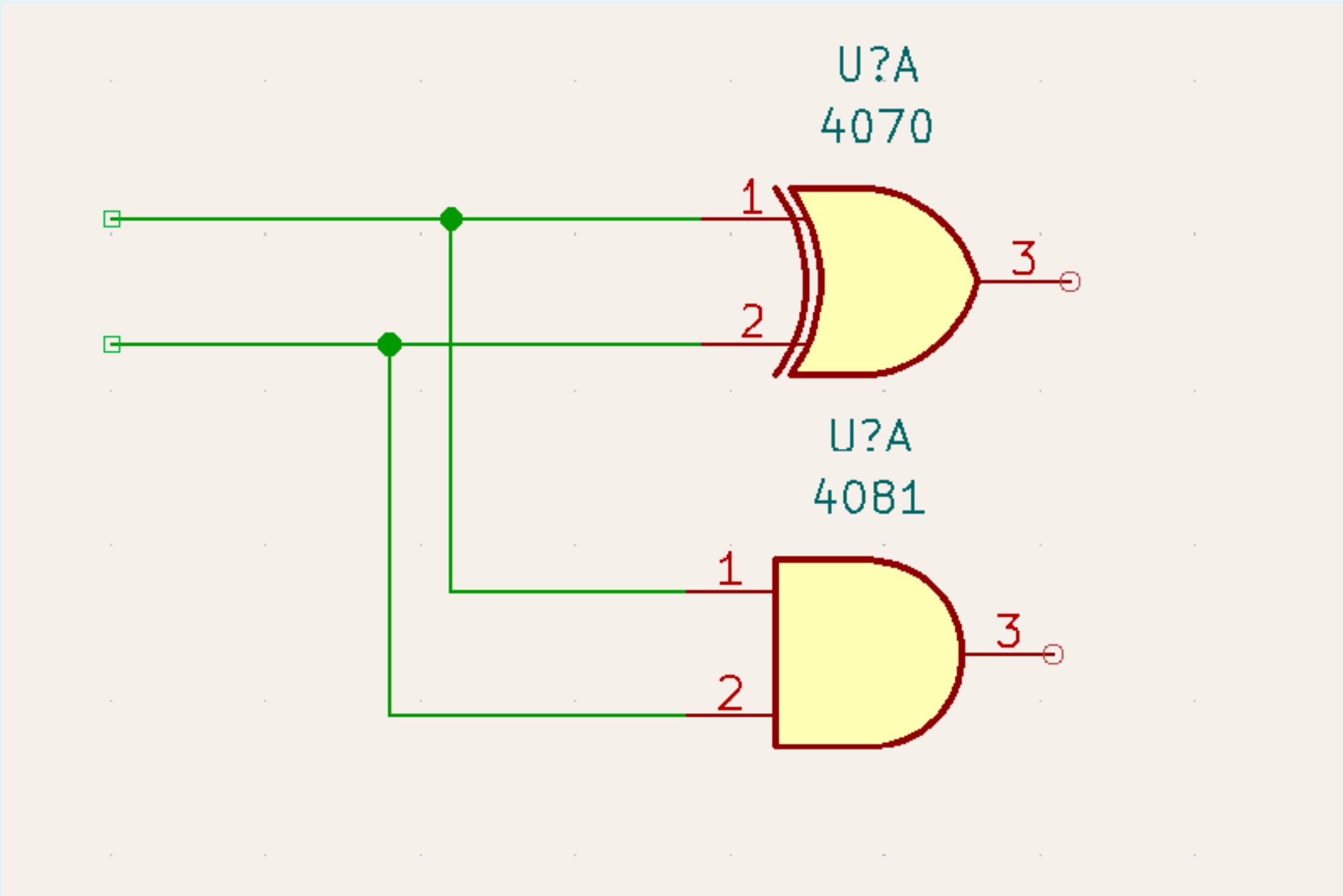


A	B	AND	XOR
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0


半加算器(一桁入力の足し算)

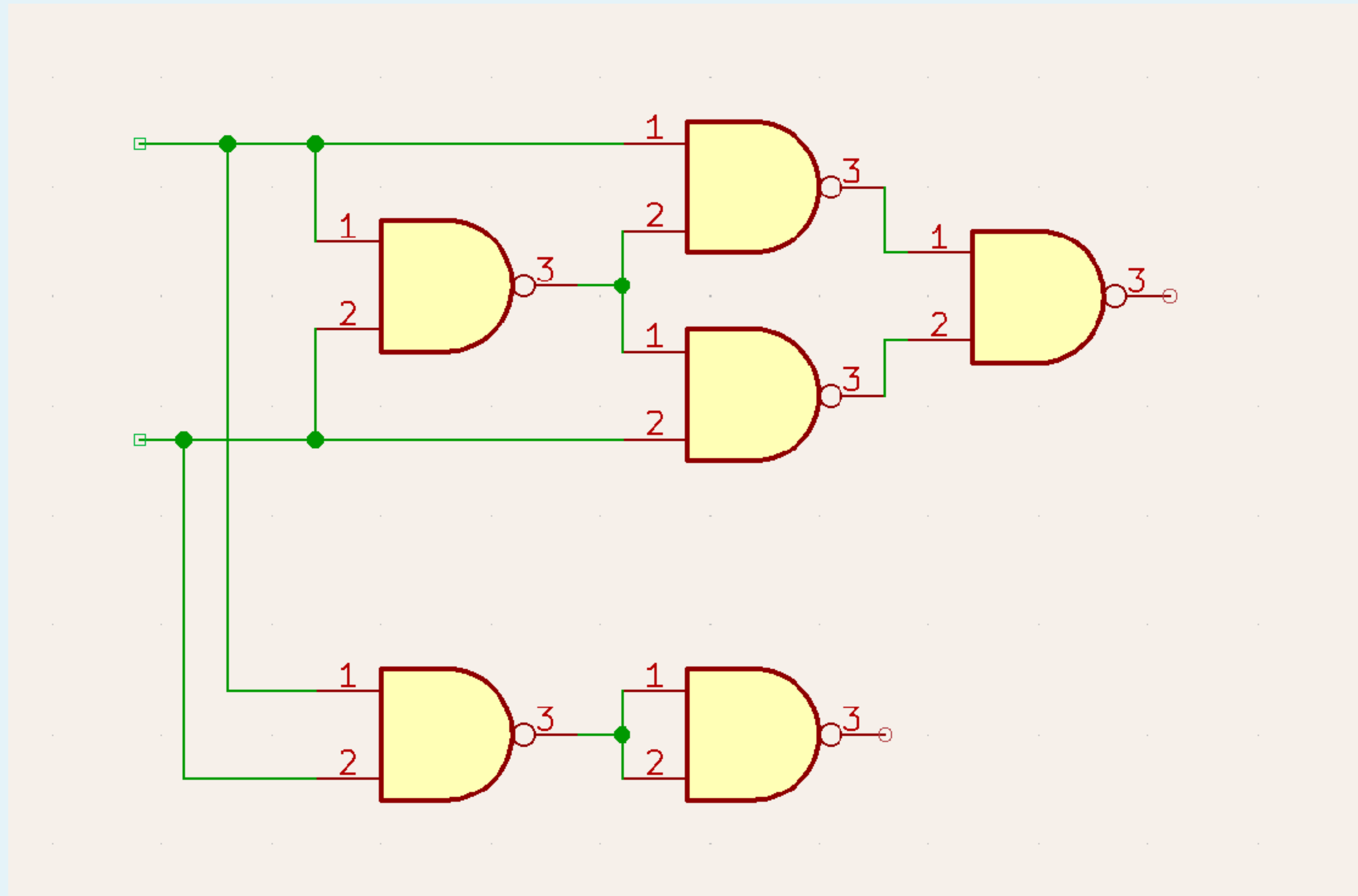


半加算器(一桁入力の足し算)

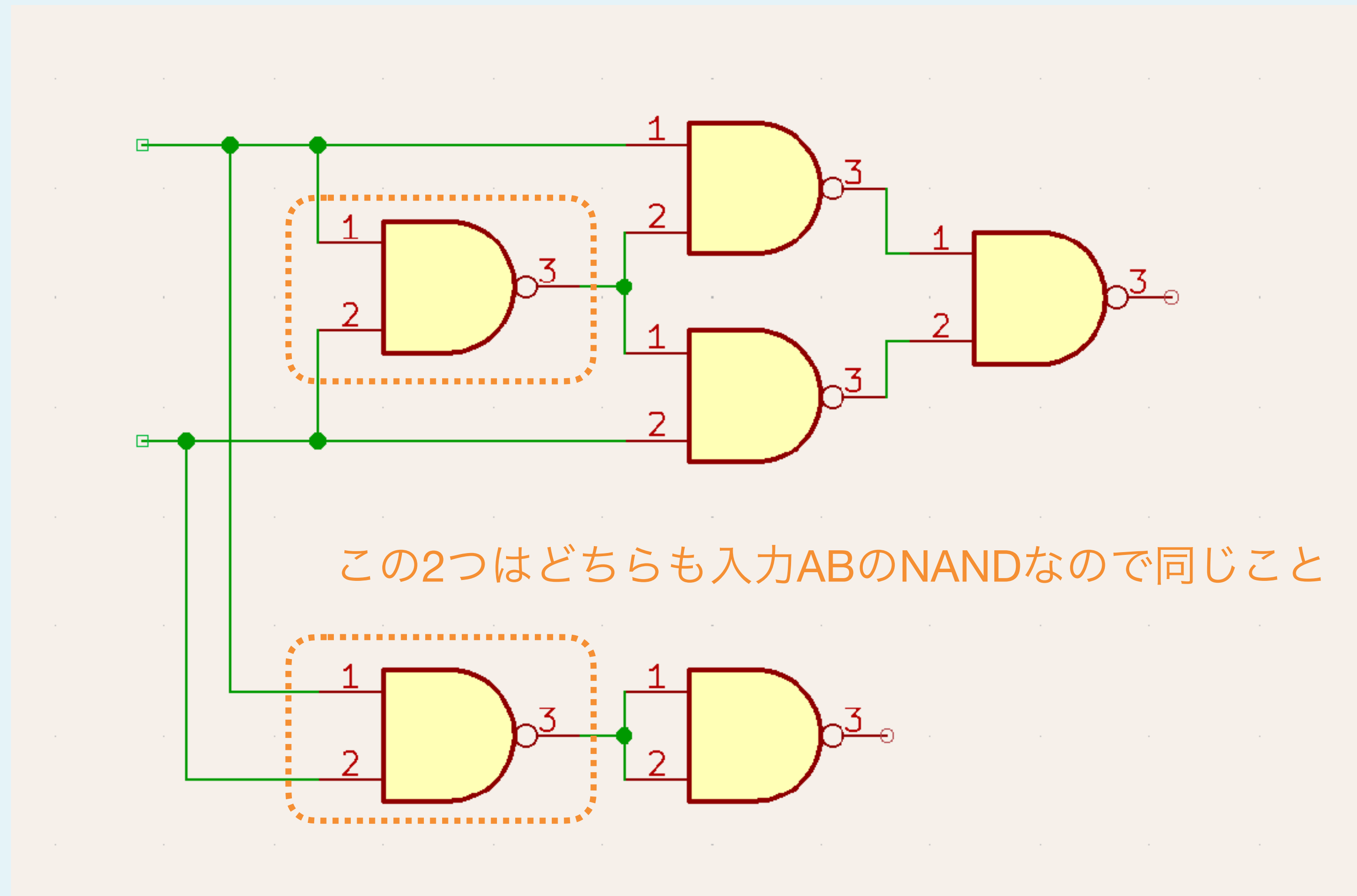


半加算器(一桁入力の足し算)

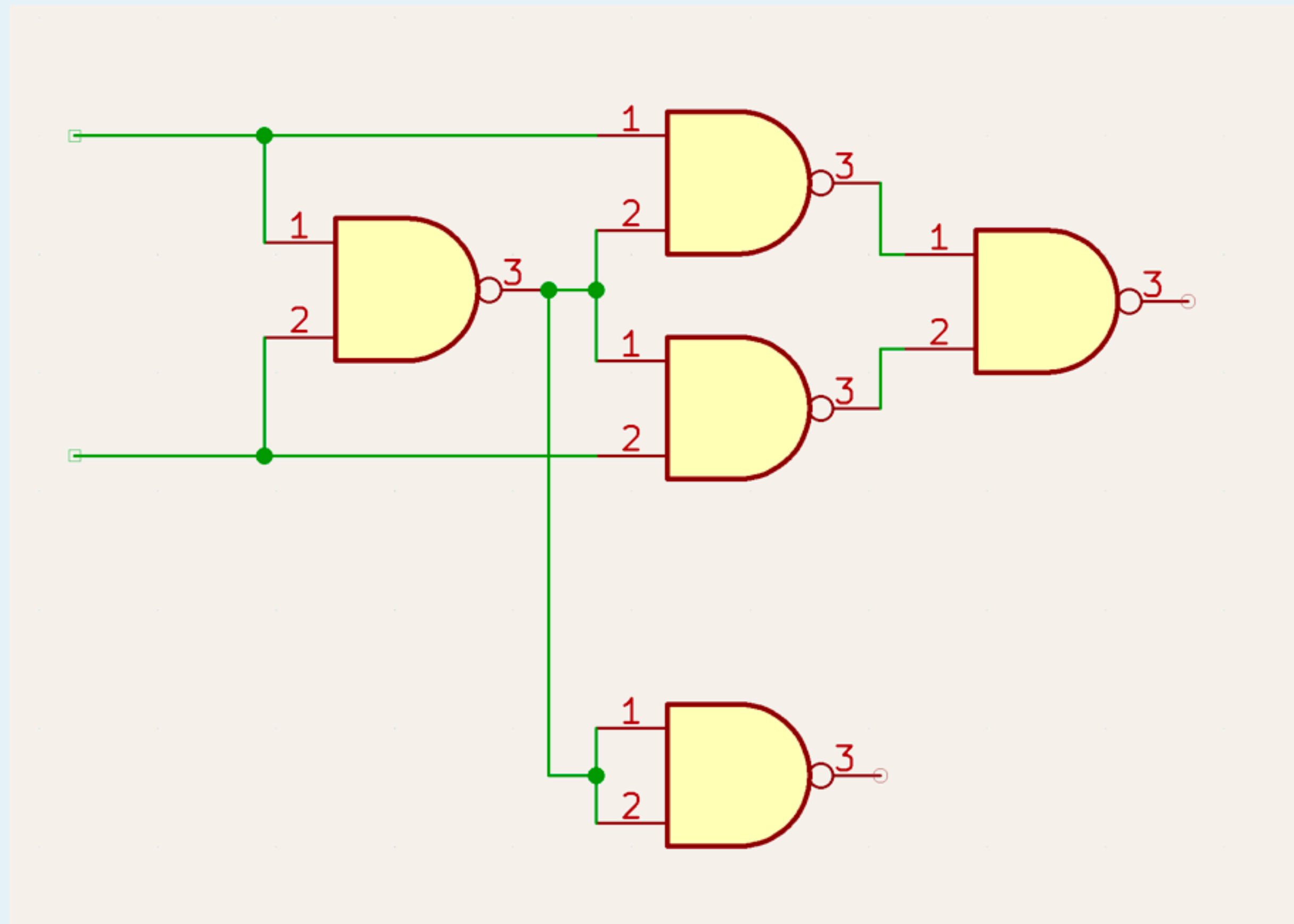

全加算器(一桁入力の足し算、桁上がり対応)

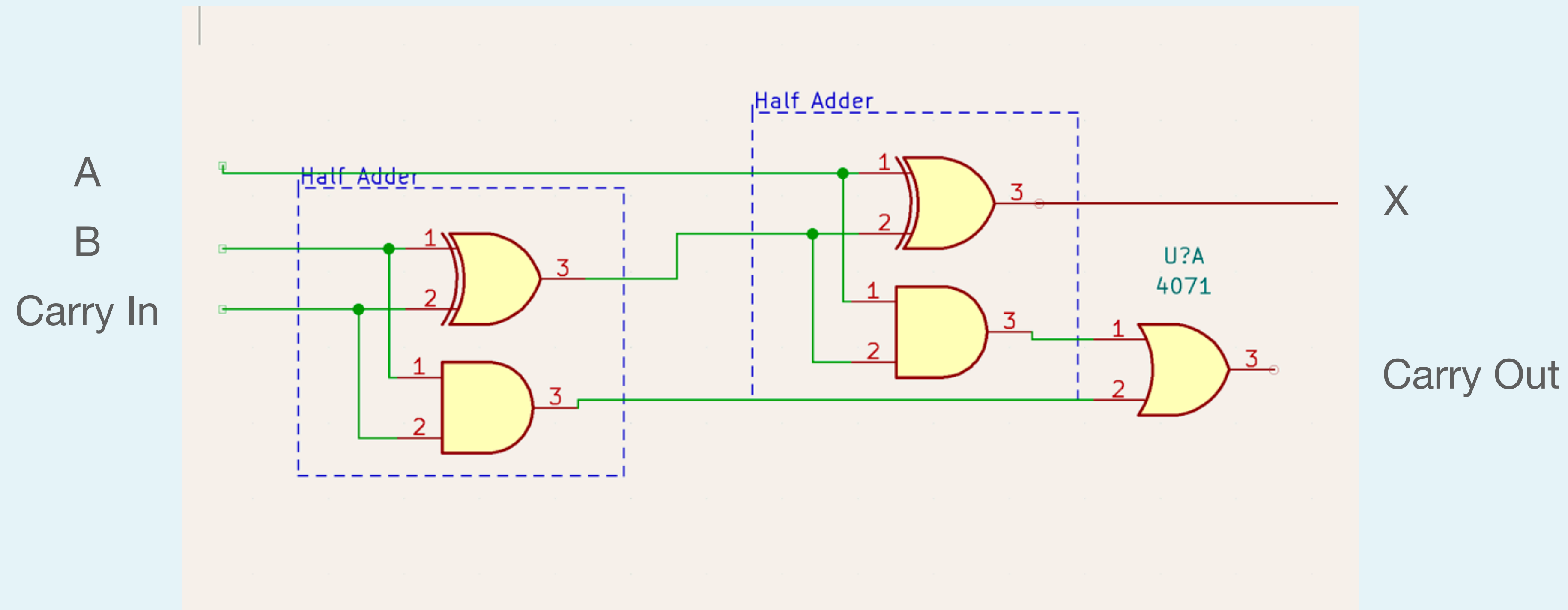

全加算器(一桁入力の足し算、桁上がり対応)

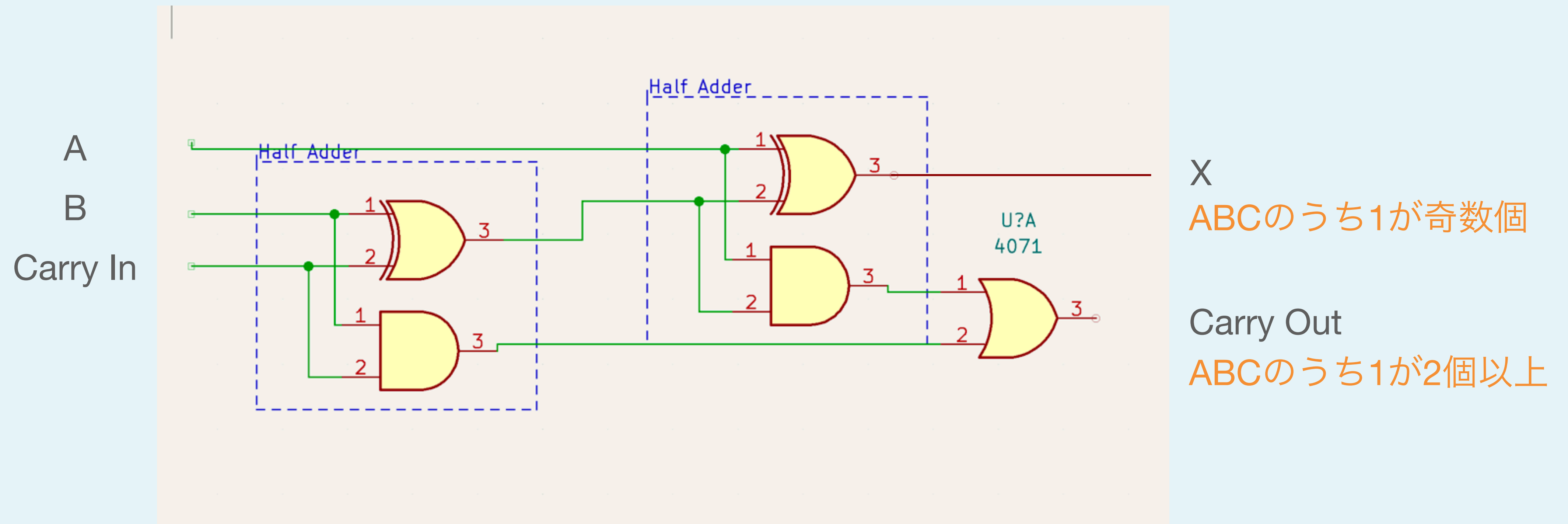

実は入力端子はどの順番に入れ替えても同じ働きをする

全加算器(一桁入力の足し算、桁上がり対応)

A
B
Carry In


A	B	Carry In	X	Carry Out
0	0	0	0	0
0	1	0	1	0
1	0	0	1	0
1	1	0	0	1
0	0	1	1	0
0	1	1	0	1
1	0	1	0	1
1	1	1	1	1

X
ABCのうち1が奇数個


Carry Out
ABCのうち1が2個以上

実は入力端子はどの順番に入れ替えても同じ働きをする


全加算器(一桁入力の足し算、桁上がり対応)

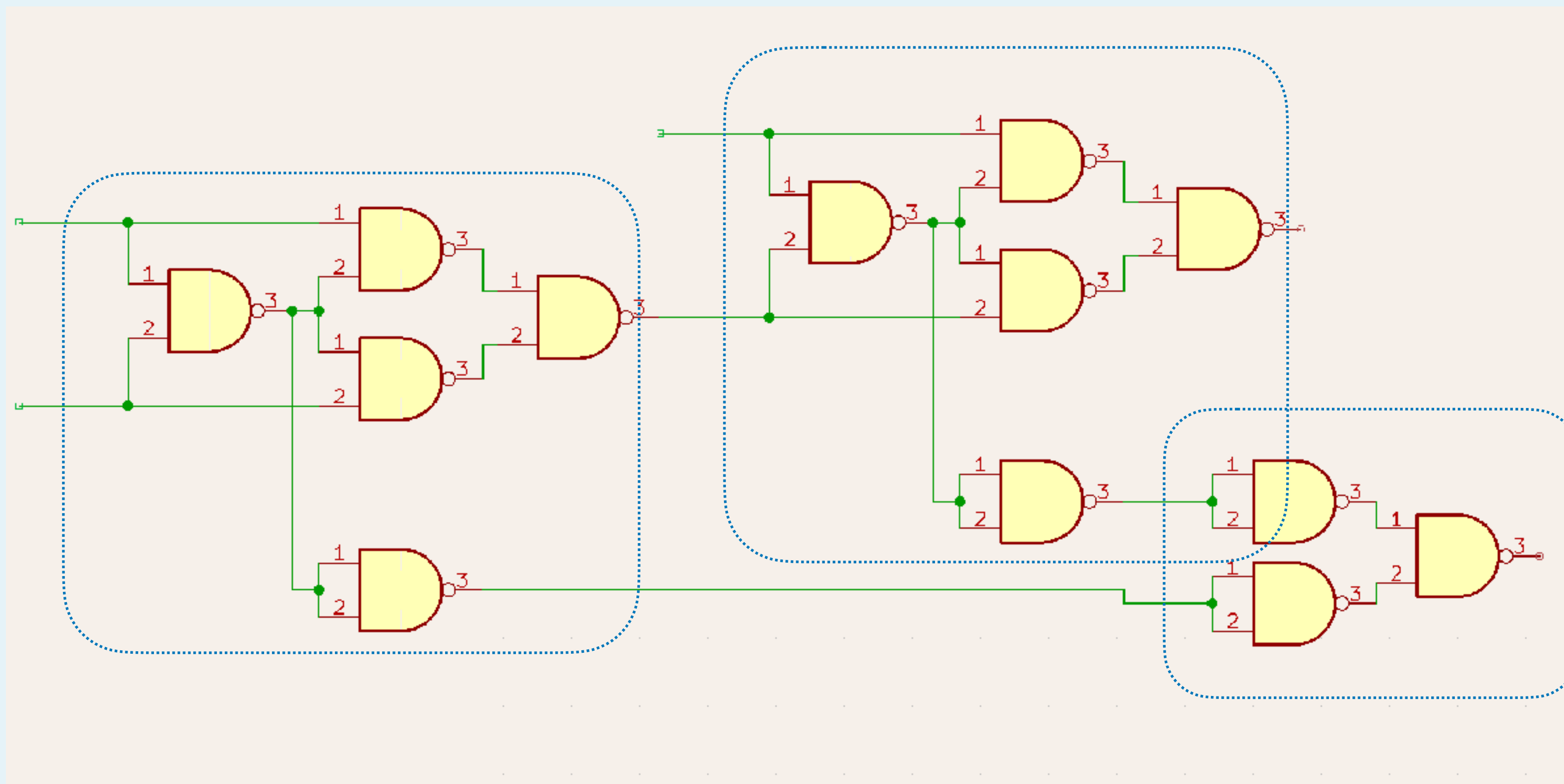


全加算器(一桁入力の足し算、桁上がり対応)


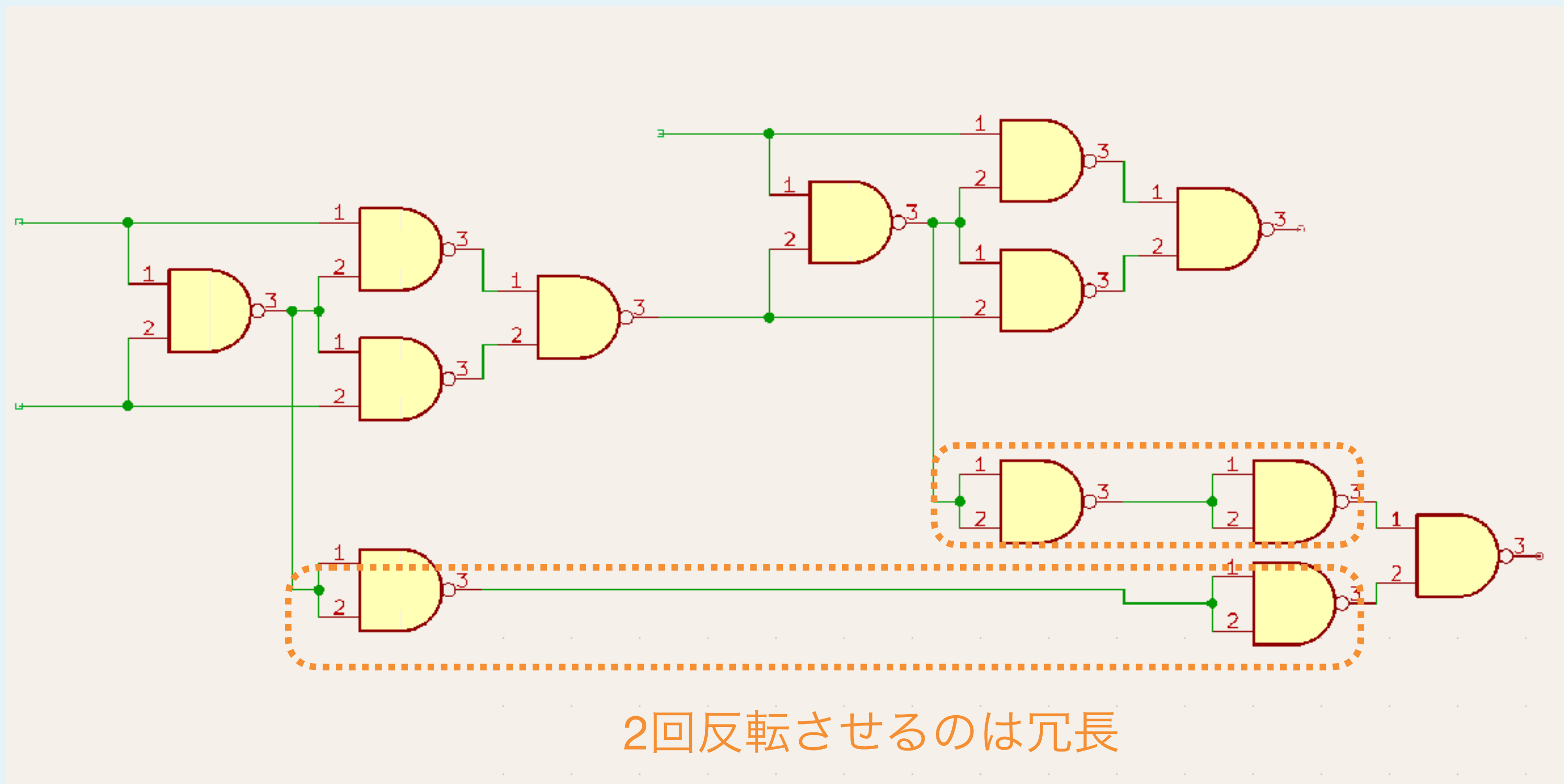


最小構成

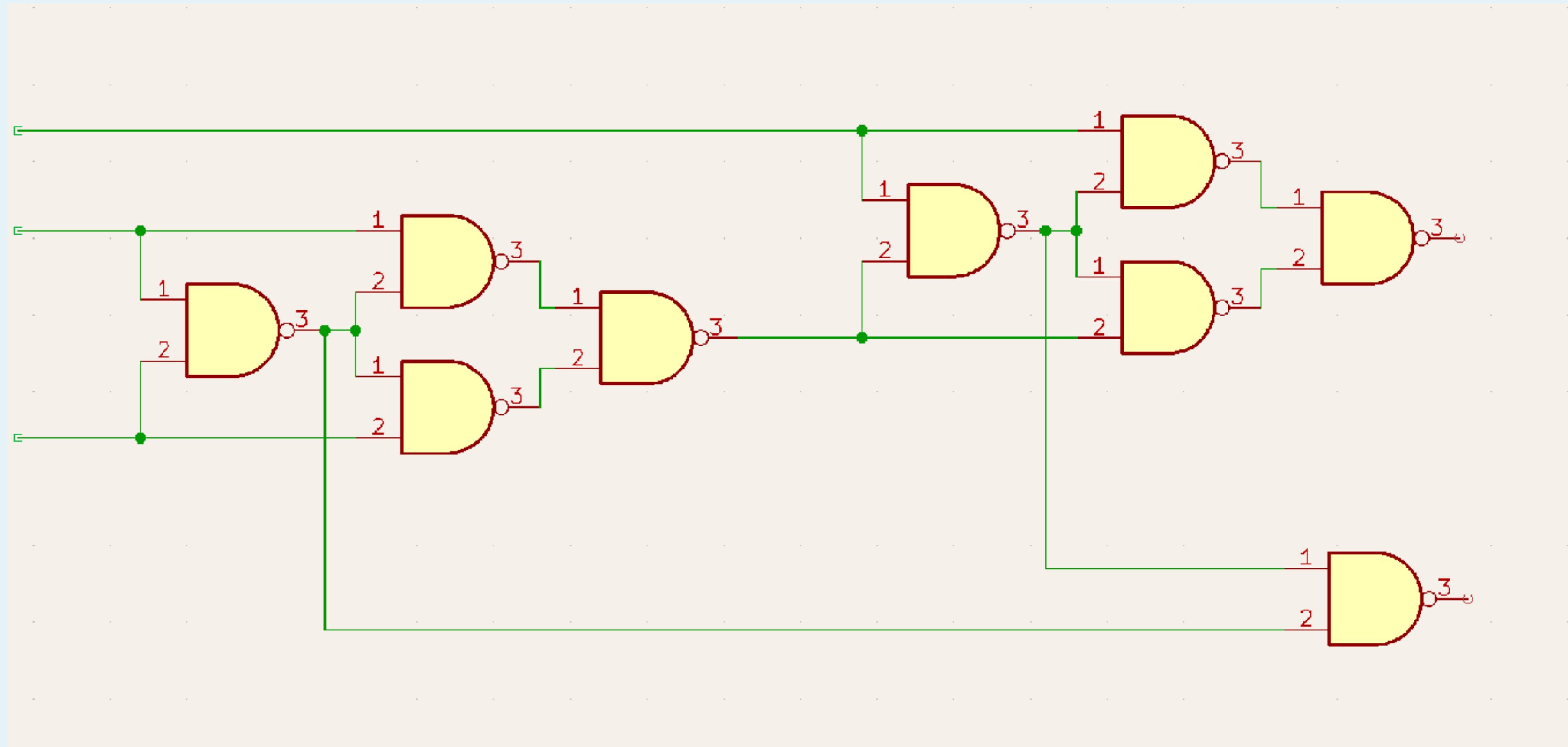

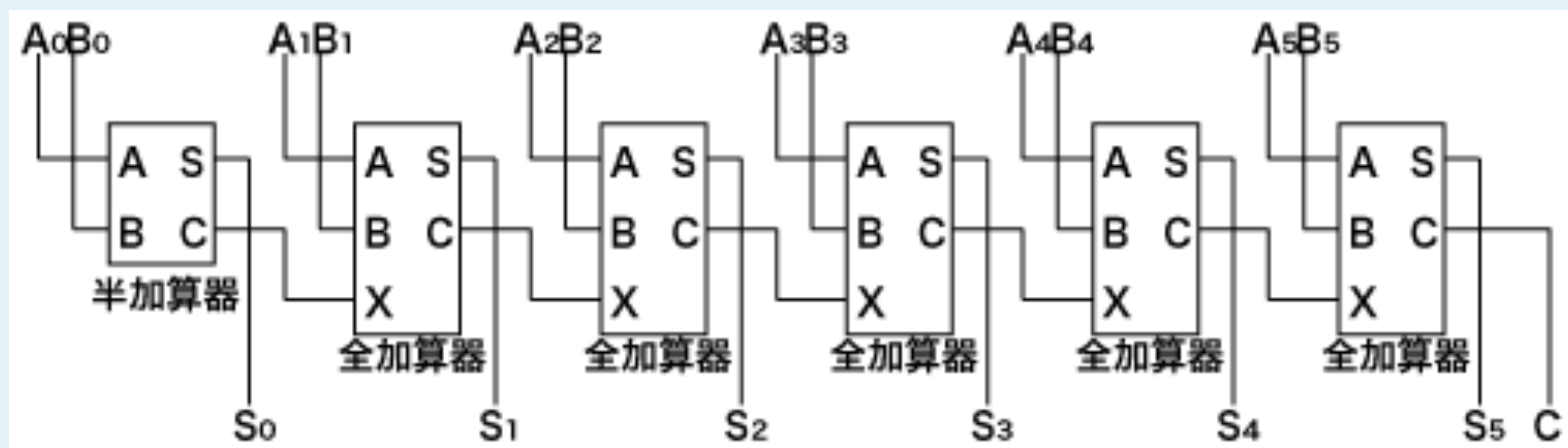

今日のゴール（14人以上いた場合は何か考える）

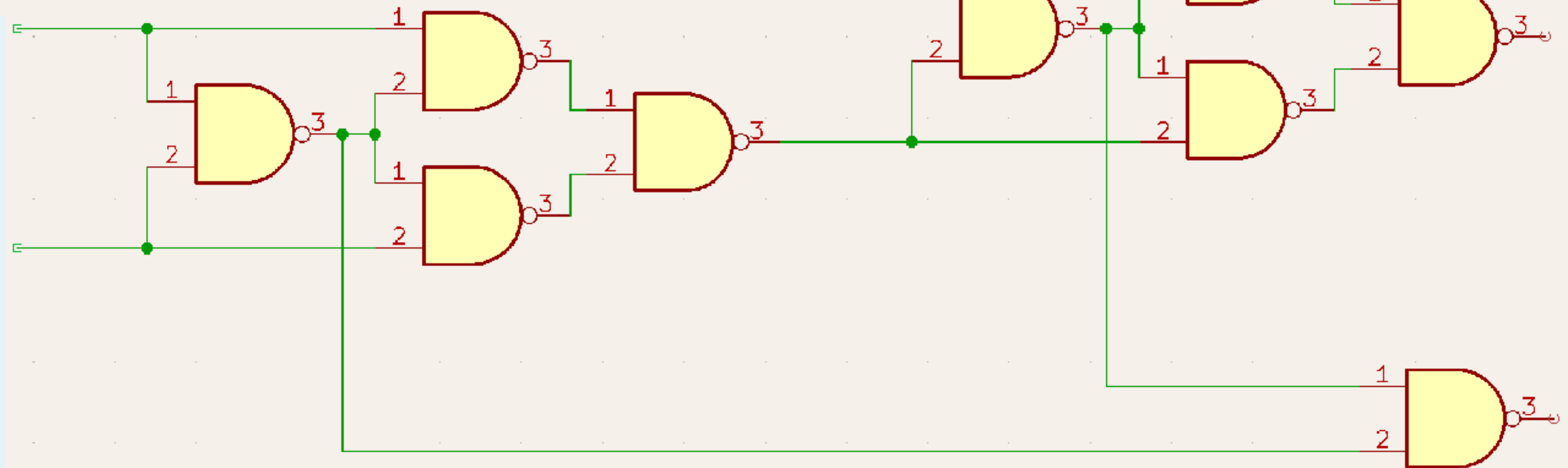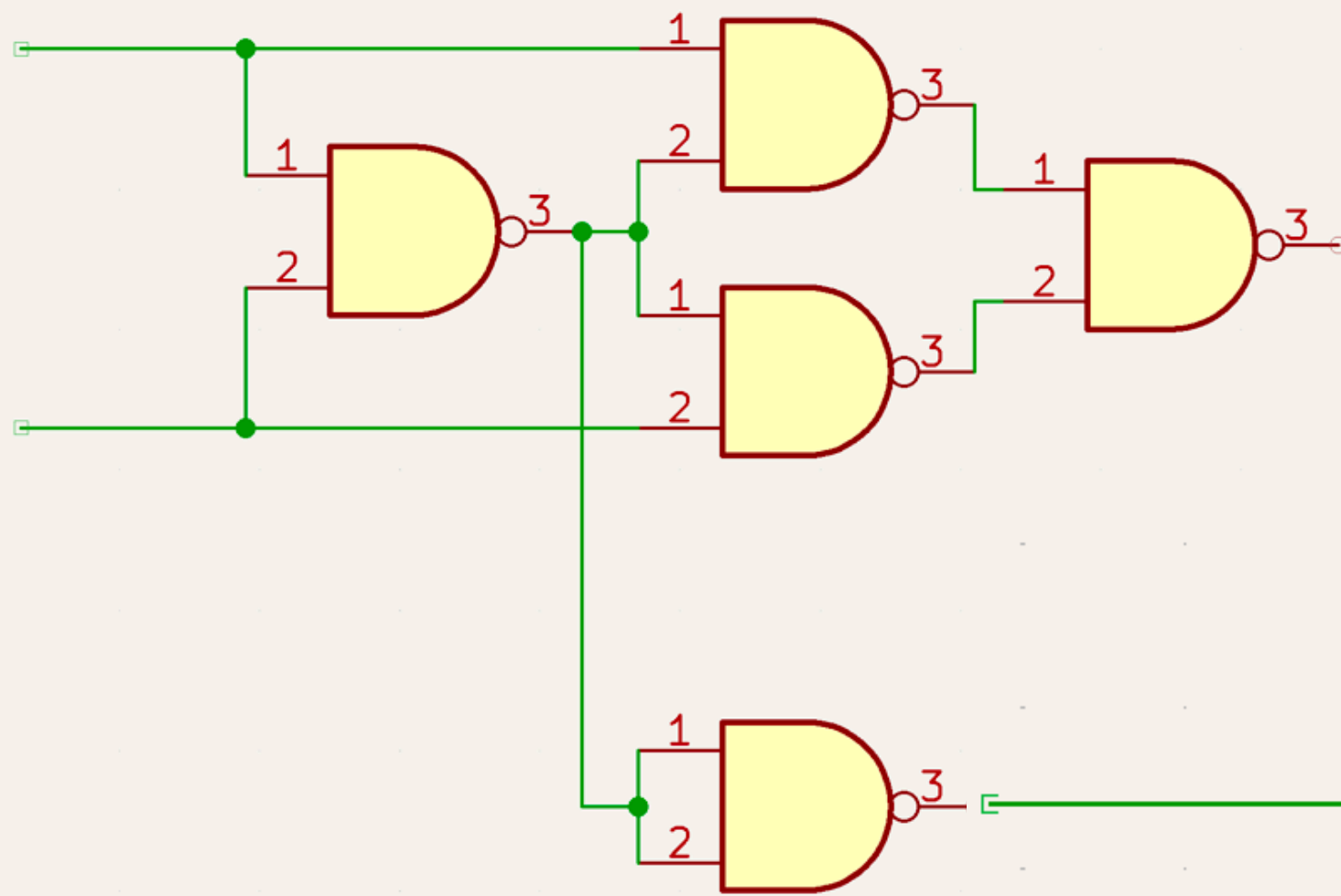





Turing Complete(LevelHead)

https://store.steampowered.com/app/1444480/Turing_Complete/

From Nand to Tetris

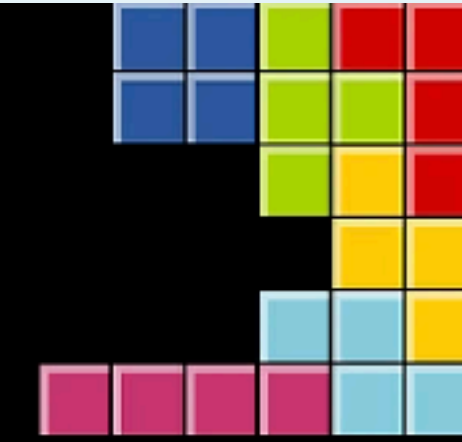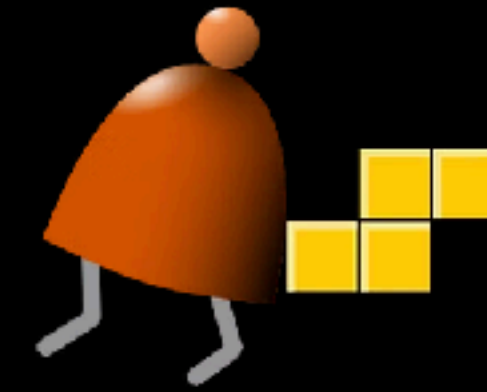Building a Modern Computer From First Principles



Home

Projects

Book

Software

Demos

License

Cool Stuff


Team

Stay in Touch

Q&A

The official website of Nand to Tetris courses

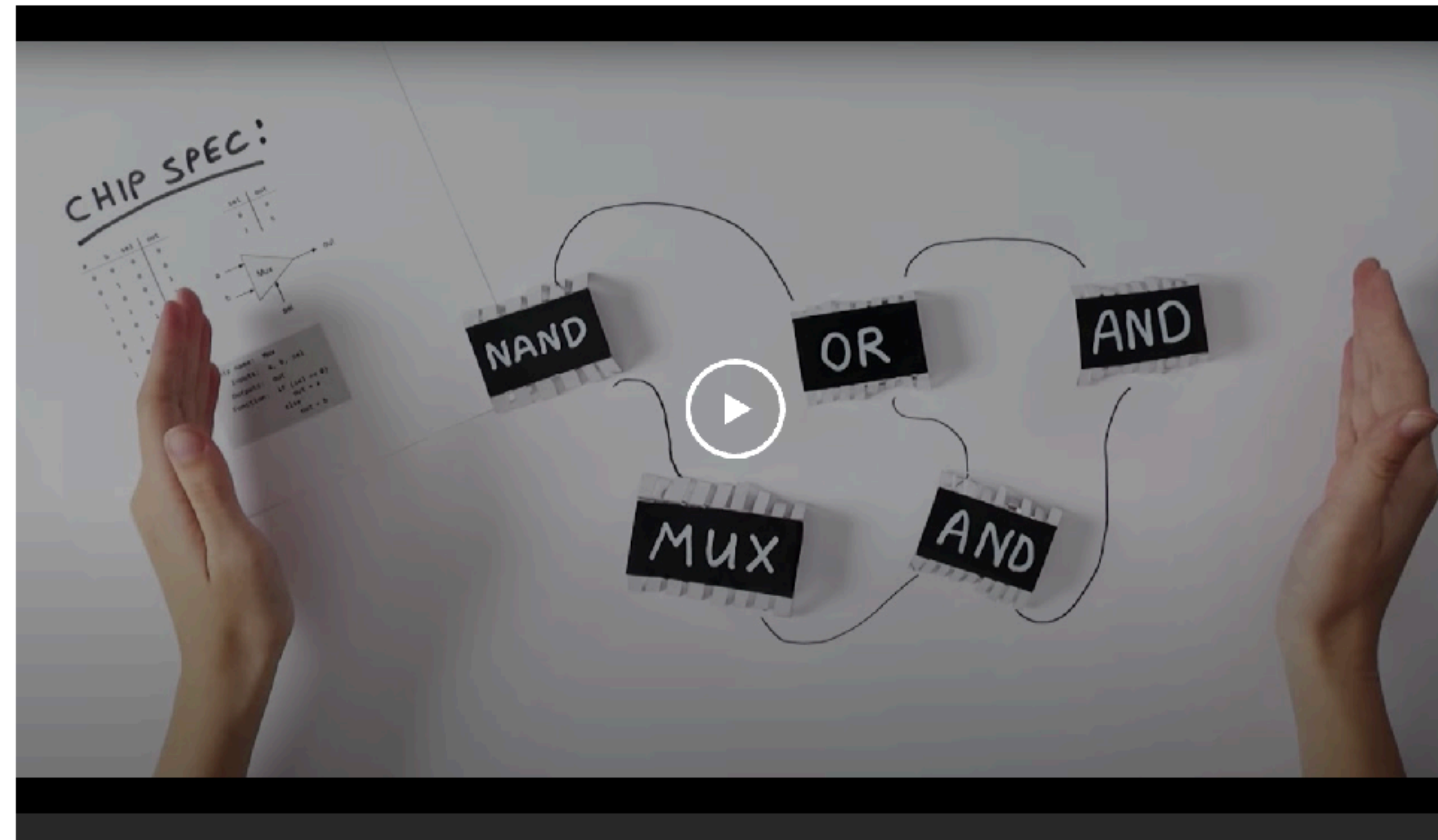And of the book [The Elements of Computing Systems](#), By [Noam Nisan](#) and [Shimon Schocken](#) (MIT Press)



<https://www.nand2tetris.org/>

O'REILLY®
Japan

BLOG

BOOKS

EBOOKS

LEARNING PLATFORM

ORDER

ABOUT

🛒

CART

コンピュータシステムの理論と実装 第2版

ーモダンなコンピュータの作り方

Noam Nisan、Shimon Schocken 著、斎藤 康毅 訳

O'REILLY®
オライリー・ジャパン

第2版

コンピュータシステムの
理論と実装

モダンなコンピュータの作り方



Noam Nisan 著
Shimon Schocken
斎藤 康毅 訳

TOPICS:

[System/Network](#)

発行年月日:
2024年12月

PRINT LENGTH:
472

ISBN:
978-4-8144-0087-4

原書:
[The Elements of Computing Systems, Second Edition](#)

FORMAT:
Print PDF EPUB
Ebook
4,400円

Print
4,400円
書籍のご注文は[オーム社サイト](#)へ

Ebookを購入する

コンピュータシステムの理論と実装 第2版 ーモダンなコンピュータの作り方

Noam Nisan、Shimon Schocken著、斎藤 康毅訳 (Nand2Tetrisの邦訳書)

<https://www.oreilly.co.jp/books/9784814400874/>

次回の予告

- マイクロコントローラ（Arduino）を使って、プログラミングと電子工作を組み合わせていきます。
- Arduino IDEを自分のコンピュータで作業したい場合のインストール方法は後日共有します